

# ENGR 065 Electric Circuits

## Lecture 16: Circuit Elements and Analysis in the $s$ Domain

# Today's Topics


- ▶ Circuit elements in the  $s$  domain
- ▶ Circuit analysis in the  $s$  domain
- ▶ Transfer functions
- ▶ Examples of circuit analysis in the  $s$  domain

Covered in Sections 13.1, 13.2, 13.3, 13.4, and 13.5

# Circuit Elements in the s Domain–Resistors

- ▶ Resistors in the time domain


$$v(t) = Ri(t) \text{ - Ohm's law}$$

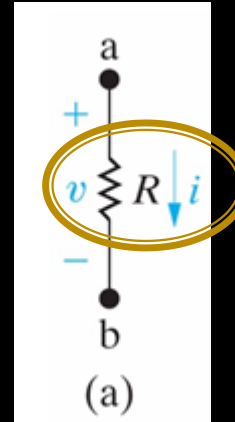

Applying Laplace transform to the above law, we have:

$$V(s) = RI(s)$$


Which is Ohm's law in the s domain

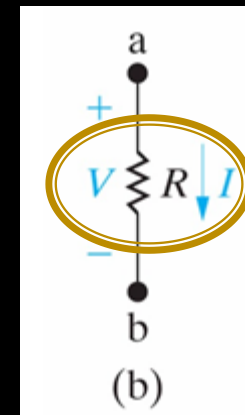


# Circuit Elements in the s Domain–Capacitors

Capacitors in the time domain

$$i(t) = C \frac{dv(t)}{dt}$$

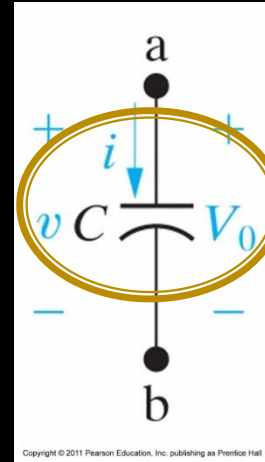

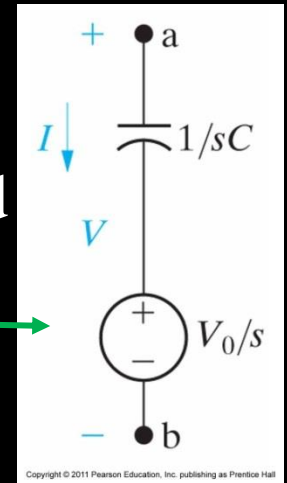
Applying the Laplace transform to the above equation and rearranging, we have:  $V(s) = \left(\frac{1}{sC}\right) I(s) + \frac{V_0}{s}$



If the initial voltage on the capacitor is zero, which is

$V_0 = 0$ , we have  $V(s) = \left(\frac{1}{sC}\right) I(s) = Z(s)I(s)$

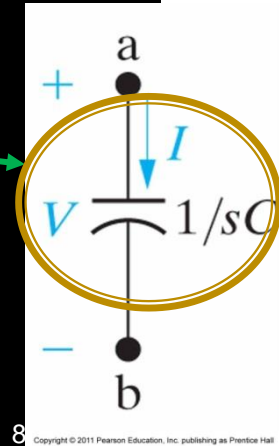
where  $Z(s) = \frac{1}{sC}$  is called impedance,  
measured in ohms



# Circuit Elements in the s Domain–Inductors


Inductors in the time domain

$$v(t) = L \frac{di(t)}{dt}$$

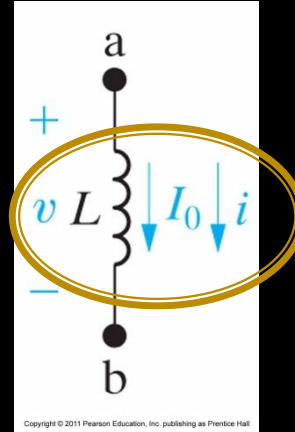

Applying the Laplace transform to the above equation and rearranging, we have:


$$V(s) = sLI(s) - LI_0$$

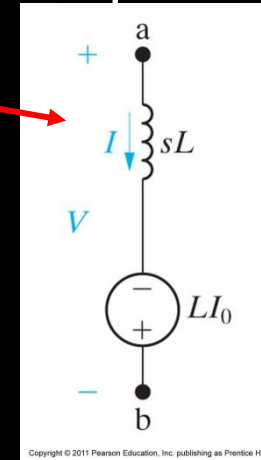

If the initial current in the inductor is zero, which is  $I_0 = 0$ , we have:

$$V(s) = sLI(s) = Z(s)I(s)$$

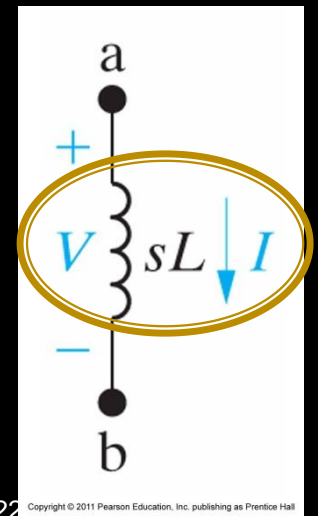where  $Z(s) = sL$  is called impedance, measured in ohms



# Circuit Analysis in the s Domain

- ▶ If the initial voltage on the capacitors and the initial current in the inductors are zero, the  $v - i$  relationship for all passive elements has the form:


$$V(s) = ZI(s) \text{ - Ohm's law in the s domain}$$

where  $Z$  refers to the s-domain impedance of elements. It has the unit of ohms ( $\Omega$ )

- ▶ All the techniques of circuit analysis developed for pure resistive circuits can be used in s-domain circuit analysis.
  1. The series-parallel simplifications
  2. KCL and KVL
  3. Source transformations
  4. Thévenin and Norton equivalents
  5. Node-voltage and mesh-current methods
  6. Superpositions (if circuits are linear)


What you need to do is to turn a circuit model in the time domain to the one in the s domain by changing  $v(t) \rightarrow V(s)$ ,  $i(t) \rightarrow I(s)$ ,  $L \rightarrow sL$ ,  $C \rightarrow \frac{1}{sC}$  and remaining  $R$  the same.
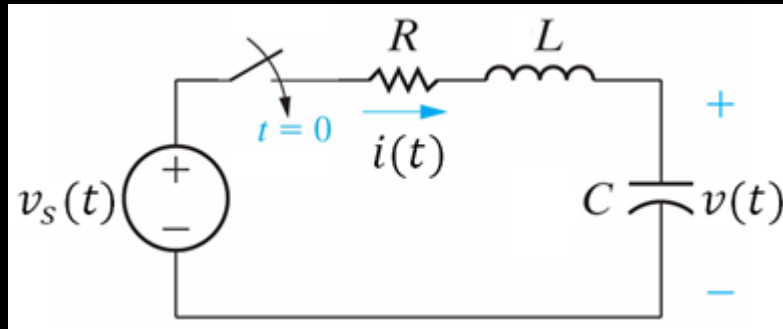
# Applications in Series- Connected RLC Circuits



The time domain

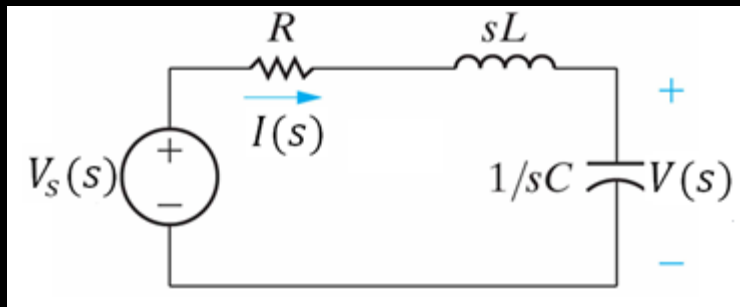If the initial energy stored in the circuit is zero. The above circuit in the s domain is



The s domain

By applying KVL to the circuit in the s domain, we have


$$RI(s) + sLI(s) + V(s) = V_s(s)$$

$$V(s) = \frac{1}{sC} I(s)$$



$$V(s) = \frac{V_s(s)/LC}{s^2 + \left(\frac{R}{L}\right)s + (1/LC)}$$
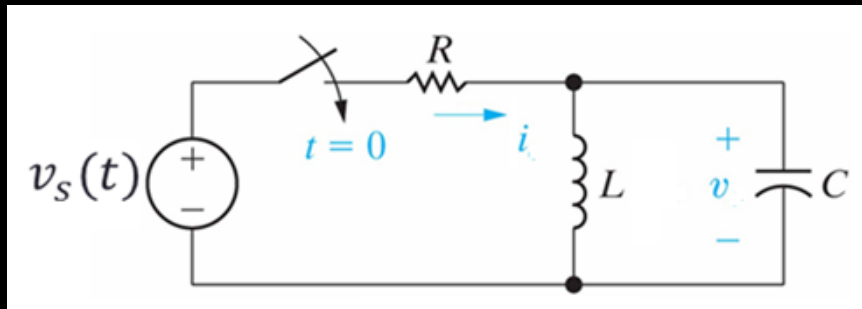
# Applications in Parallel-Connected RLC Circuits




The time domain

Node-Voltage method:

$$\frac{V(s) - V_s(s)}{R} + \frac{V(s)}{sL} + \frac{V(s)}{\frac{1}{sC}} = 0$$


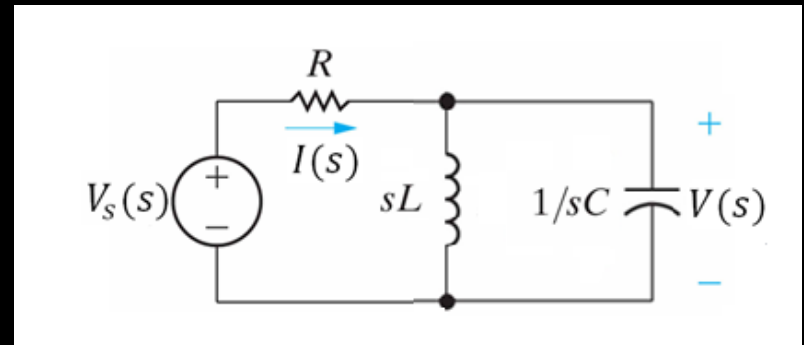
$$V(s) = \frac{sV_s(s)/RC}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)}$$



The s domain

$$I(s) = \frac{V_s(s) - V(s)}{R}$$

$$\text{or } I(s) = \frac{V(s)}{sL} + \frac{V(s)}{\frac{1}{sC}}$$



$$I(s) = \frac{V_s(s)\left(\frac{1}{R}s^2 + \frac{1}{RLC}\right)}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)}$$



# The Transfer Function


The transfer (system) function is the ratio of the output(response) to the input(source) in the frequency (s) domain. There are two premises: the circuit

1. is a linear time-invariant circuit
2. has zero initial conditions

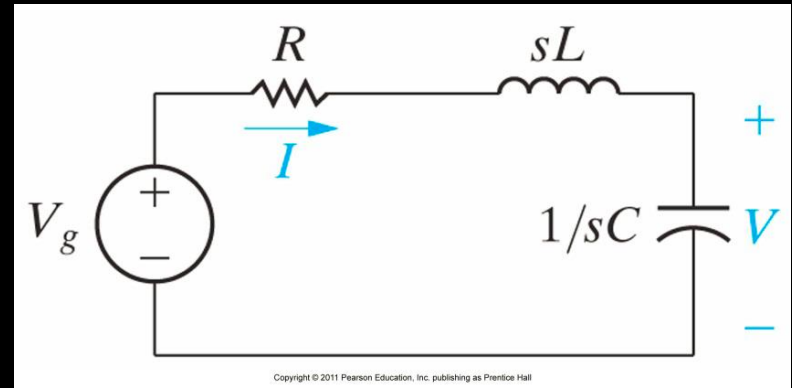Examples:



$$H(s) = \frac{V(s)}{V_g(s)} = \frac{1/LC}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$H(s) = \frac{I(s)}{V_g(s)} = \frac{\frac{1}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



# Example #1 (P.493)

Example 1: (P. 493)

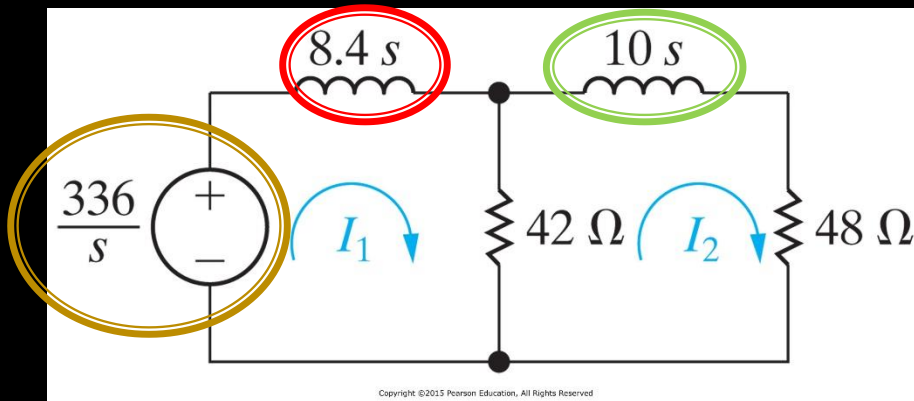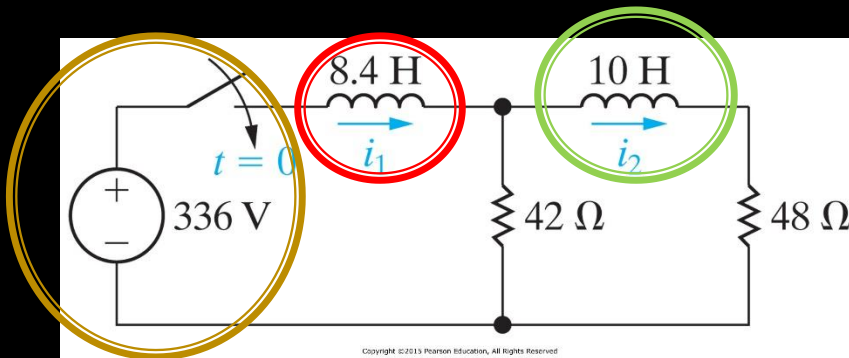

Mesh-current method:

$$(42 + 8.4s)I_1 - 42I_2 = \frac{336}{s}$$

$$-42I_1 + (90 + 10s)I_2 = 0$$

$$\Delta = \begin{vmatrix} 42 + 8.4s & -42 \\ -42 & 90 + 10s \end{vmatrix}$$

$$N_1 = \begin{vmatrix} \frac{336}{s} & -42 \\ 0 & 90 + 10s \end{vmatrix}$$

$$N_2 = \begin{vmatrix} 42 + 8.4s & \frac{336}{s} \\ -42 & 0 \end{vmatrix}$$

No initial energy. Find the step responses of  $i_1(t)$  and  $i_2(t)$ .

# Example #1 (P.493) –cont'd

$$I_1 = \frac{N_1}{\Delta} = \frac{40(s+9)}{s(s+2)(s+12)} \qquad I_2 = \frac{N_2}{\Delta} = \frac{168}{s(s+2)(s+12)}$$

$$I_1 = \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+12} = \frac{15}{s} - \frac{14}{s+2} - \frac{1}{s+12}$$

⇒  $i_1(t) = (15 - 14e^{-2t} - e^{-12t})u(t)$




$$I_2 = \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+12} = \frac{7}{s} - \frac{8.4}{s+2} + \frac{1.4}{s+12}$$

⇒  $i_2(t) = (7 - 8.4e^{-2t} + 1.4e^{-12t})u(t)$

# Steps of Circuit Analysis in the $s$ Domain

1. Check the initial energy in a circuit.
2. Apply the Laplace transform to the elements and sources in the circuit.
3. Redraw the circuit in the  $s$  domain.
4. Use the circuit analysis techniques discussed in the first four chapters to find the voltages/currents in the  $s$  domain.
5. Expand the voltages/currents into a sum of partial fractions.
6. Apply the inverse Laplace transform and find the voltages/currents in the time domain.
7. Use the initial-value and final-value theorems to verify the solutions found in step 6.


# Example #2 (P.495)

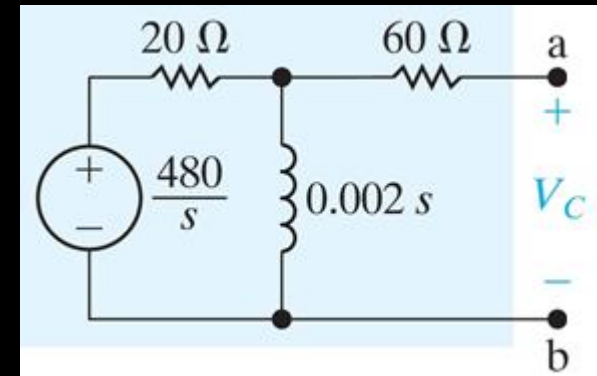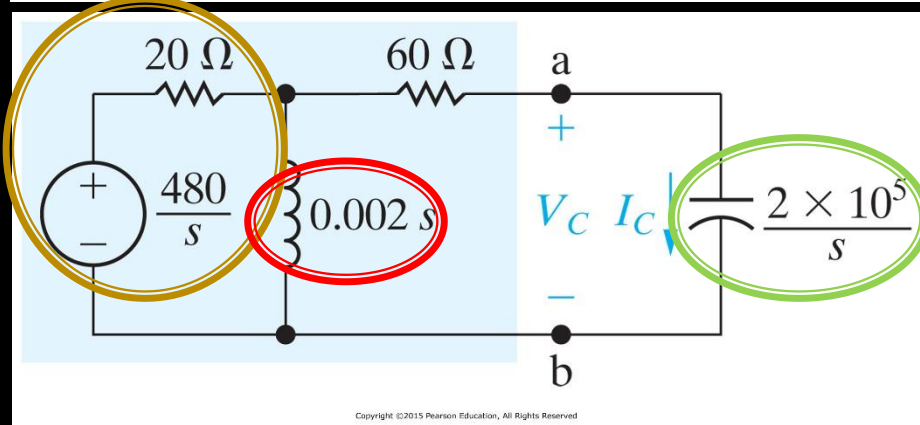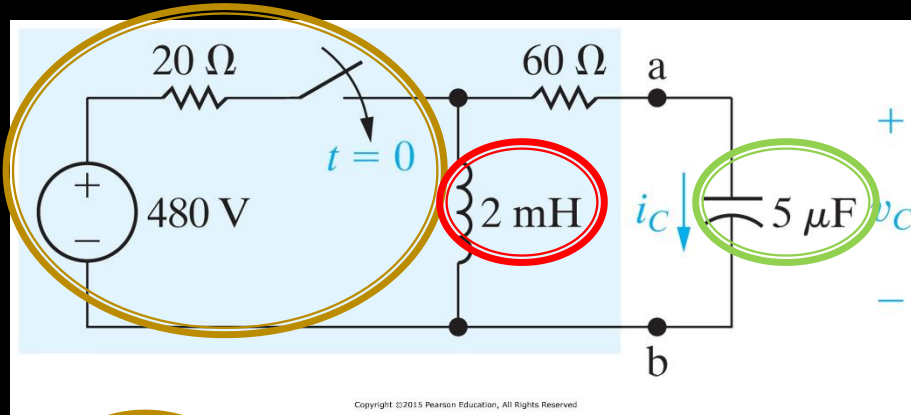

No initial energy. Use Thévenin equivalent to find  $i_c(t)$ .


$$V_{Th} = \frac{(480/s)(0.002s)}{20 + 0.002s} = \frac{480}{s + 10^4}$$

# Example #2 (P.495) – cont'd

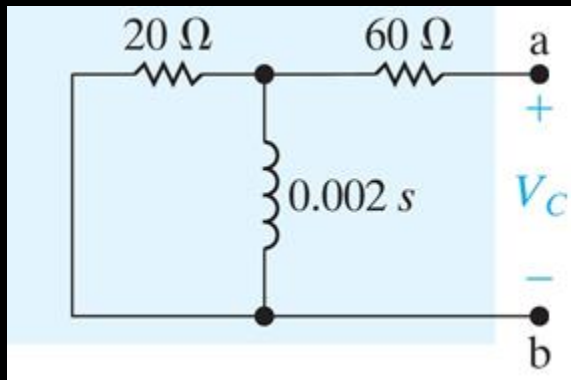

$$Z_{Th} = 60 + \frac{0.002s(20)}{20 + 0.002s} = \frac{80(s + 7500)}{s + 10^4}$$
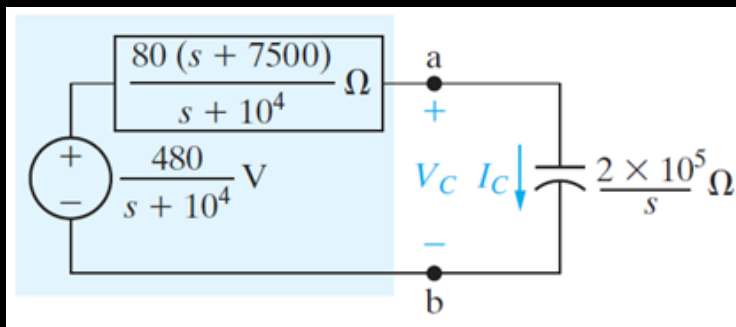
$$I_c(s) = \frac{\frac{480}{s + 10^4}}{\frac{80(s + 7500)}{s + 10^4} + \frac{2 \times 10^5}{s}} = \frac{6s}{(s + 5000)^2}$$



$$I_c(s) = \frac{k_1}{(s + 5000)^2} + \frac{k_2}{s + 5000} = \frac{-30,000}{(s + 5000)^2} + \frac{6}{s + 5000}$$

$$i_c(t) = (-30,000te^{-5000t} + 6e^{-5000t})u(t) \text{ A}$$

# Summary

- ▶ The Laplace transform of the voltage - current equation for each element:
  - a. Resistors:  $V(s) = RI(s)$
  - b. Inductors:  $V(s) = sLI(s) - LI_0$
  - c. Capacitors:  $V(s) = \left(\frac{1}{sC}\right) I(s) - V_0/s$
- ▶ Several examples of circuits analysis in the s domain are given in this lecture.
  - a. How to find the transfer function of a circuit.
  - b. How to use circuit elements in the s domain to build a circuit model.
  - c. How to apply circuit analysis techniques to solve the quantities for a circuit in which inductors and capacitors are included.

In next lecture, we will discuss the steady-state sinusoidal response