

Homework 6

Answer all the required problems for each assignment and round your final solutions to two decimal places, if needed.

Assignment 1

(Around your solutions to two decimal places if necessary)

1. Determine the inverse Laplace transform of each of the following functions. **(9 pts/each = 81 pts)**

a. $F(s) = \frac{1}{s} + \frac{2}{s+1}$

b. $F(s) = \frac{e^{-4s}}{s+2}$

c. $F(s) = \frac{3s+1}{s+4}$

d. $F(s) = \frac{4}{(s+1)(s+3)}$

e. $F(s) = \frac{6s}{(s+1)(s+2)}$

f. $F(s) = \frac{s^2+2}{s^3+2s^2+2s}$

g. $F(s) = \frac{10}{(s+1)(s^2+4s+8)}$

h. $F(s) = \frac{2}{s(s+1)^2}$

i. $F(s) = \frac{8}{s(s+1)^3}$


2. Given that $v(0^-) = 5$, $v'(0^-) = 10$, solve the following equation for the $v(t)$. **(19 pts)**

$$\frac{d^2v(t)}{dt^2} + 5\frac{dv(t)}{dt} + 6v(t) = 25e^{-t}u(t)$$

Assignment 2


(Around your solutions to two decimal places if necessary)

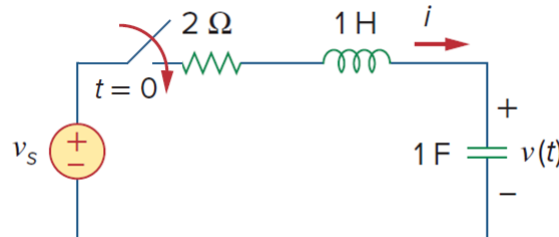1. The initial energy stored in the following circuit is zero. The switch is closed at $t = 0$. Assume $V(s) = \mathcal{L}\{v(t)\}$ and $I(s) = \mathcal{L}\{i(t)\}$. **(50 pts)**



If $v_s(t) = 10\text{ V}$,

- Write the differential equations in terms of $v(t)$ and $i(t)$.
 - Find $V(s)$ and $I(s)$.
 - Find $v(t)$ and $i(t)$.
 - Find zeros and poles of $V(s)$ and $I(s)$.
 - Use the initial value theorem to find $v(0^+)$ and $i(0^+)$ from $V(s)$ and $I(s)$.
 - Use the final value theorem to find $v(\infty)$ and $i(\infty)$ from $V(s)$ and $I(s)$.
 - Do your answers in (e) and (f) make sense in the terms of the above circuit behavior? Please explain.
2. The initial energy stored in the following circuit is zero. The switch is closed at $t = 0$. Assume $V(s) = \mathcal{L}\{v(t)\}$ and $I(s) = \mathcal{L}\{i(t)\}$. **(50 pts)**

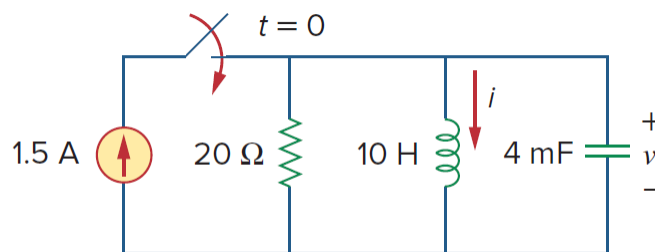


- Write the differential equations in terms of $v(t)$ and $i(t)$.
- Find $V(s)$ and $I(s)$.
- Find $v(t)$ and $i(t)$.
- Find zeros and poles of $V(s)$ and $I(s)$.
- Use the initial value theorem to find $v(0^+)$ and $i(0^+)$ from $V(s)$ and $I(s)$.
- Use the final value theorem to find $v(\infty)$ and $i(\infty)$ from $V(s)$ and $I(s)$.

- g. Do your answers in (e) and (f) make sense in the terms of the above circuit behavior? Please explain.


Assignment 3

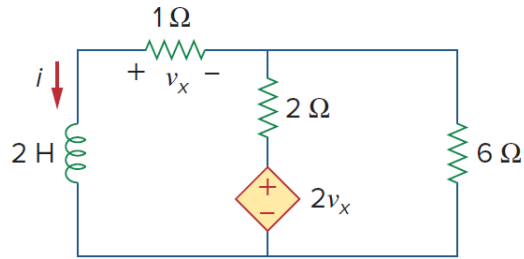1. Find $i(t)$ and $v_x(t)$ in the circuit below. Assume $I_0 = i(0^-) = 12 \text{ A}$. (20 pts)




Answer: $i(t) = 12e^{-2t} \text{ A}$, $v_x(t) = -12e^{-2t} \text{ V}$ for $t > 0$.

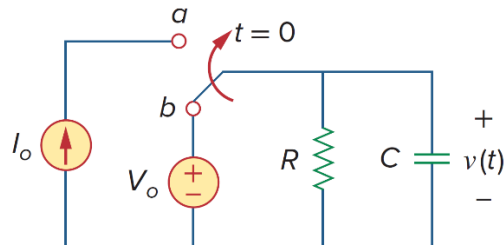2. The switch in the following circuit has been in position **b** for a long time. It is moved to position **a** at $t = 0$. Determine $v(t)$ for $t > 0$. (25 pts)



Answer: $v(t) = (V_0 - I_0 R)e^{-\frac{t}{\tau}} + I_0 R$, $t > 0$, where $\tau = RC$.

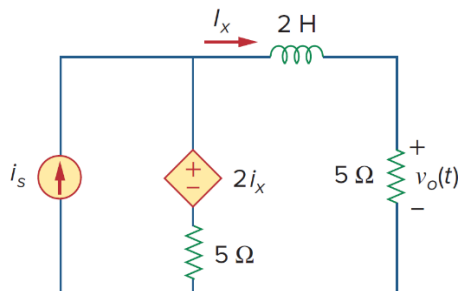3. Assume there is no initial energy stored in the circuit below at $t = 0$ and that $i_s = 10 u(t) \text{ A}$. (30 pts)



- a. Use Thevenin's theorem to find $V_o(s)$.

(Hints: Remove 5Ω resistor and find $V_{Th} = V_{oc}$. Short 5Ω resistor to find I_{sc} by using the node-voltage method, then $Z_{Th} = \frac{V_{Th}}{I_{sc}}$.)


- b. Find the transfer function of $H(s) = \frac{V_o(s)}{I_s(s)}$
 c. Applying the initial- and final- value theorems to find $v_o(0^+)$ and $v_o(\infty)$.
 d. Determine $v_o(t)$.

e. If $i_s = 20 \cos(4t + 30^\circ) u(t)$ A, determine the steady-state response $v_{oss}(t)$.

Answer: $v_o(t) = 31.25(1 - e^{-4t})u(t)$ V; $v_{oss}(t) = 31.25\sqrt{2} \cos(4t - 15^\circ)$ V

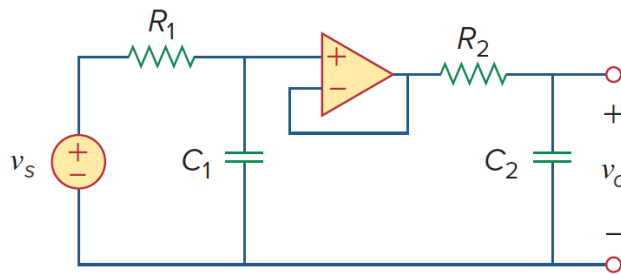4. In the op-amp circuit below, $v_s(t) = 10u(t)$. Assume that $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = 20 \text{ }\mu\text{F}$, and $C_2 = 100 \text{ }\mu\text{F}$. The op-amp in the circuit is ideal. The initial energy stored in the circuit is zero. **(25 pts)**

- Find the transfer function $H(s) = \frac{V_o(s)}{V_s(s)}$.
- Determine the type of the circuit response based on the transfer function.
- Determine $v_o(t)$ for $t > 0$.



Answer: $v_o(t) = (10 - 12.5e^{-t} + 2.5e^{-5t})u(t)$ V