

# ENGR 65 Electric Circuits

## Lecture 14: Inverse Laplace Transform and RC, RL, and RLC Circuits

# Today's Topics


- ▶ The review of complex numbers and their operations
- ▶ The inverse Laplace transform
  1. Rational functions
    - a. Proper rational functions
    - b. Improper rational functions
  2. The partial fraction expansion
- ▶ The applications of the Laplace transform in first-order RC/RL circuits and second-order RLC circuits
- ▶ The topics covered in Sections 12.6 and 12.7

# Complex Number Notation

There are two ways to describe a complex number

- Rectangular form:  $c = a + jb$
- Polar form:  $c = re^{j\theta} = r\angle\theta^0$
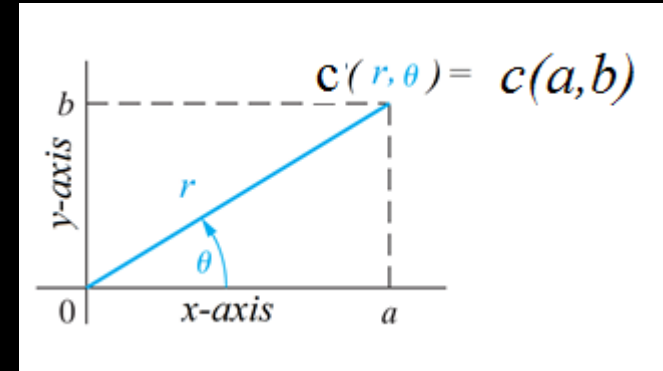
$$a = r \cos \theta$$
$$b = r \sin \theta$$





$$\begin{cases} a^2 + b^2 = r^2 \\ \tan \theta = \frac{b}{a} \end{cases} \quad \Rightarrow \quad \begin{cases} r = \sqrt{a^2 + b^2} \\ \theta = \tan^{-1}\left(\frac{b}{a}\right) \end{cases}$$
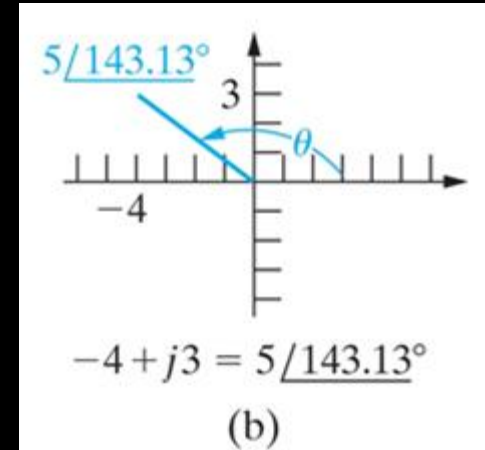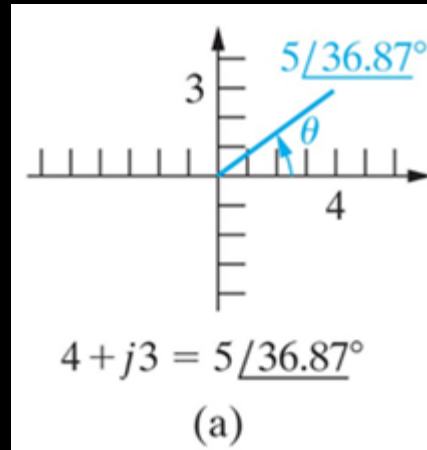
# Some Examples

$$c = a + jb = 4 + j3$$

$$\begin{cases} r = \sqrt{a^2 + b^2} = \sqrt{3^2 + 4^2} = 5 \\ \theta = \tan^{-1}\left(\frac{b}{a}\right) = \tan^{-1}\frac{3}{4} = 36.87^\circ \end{cases}$$




$$143.13^\circ = 180^\circ - 36.87^\circ$$

a)  $c = 4 + j3 = 5e^{j36.87^\circ}$


b)  $c = -4 + j3 = 5e^{j143.13^\circ}$

c)  $c = -4 - j3 = 5e^{-j143.13^\circ}$

d)  $c = 4 - j3 = 5e^{-j36.87^\circ}$

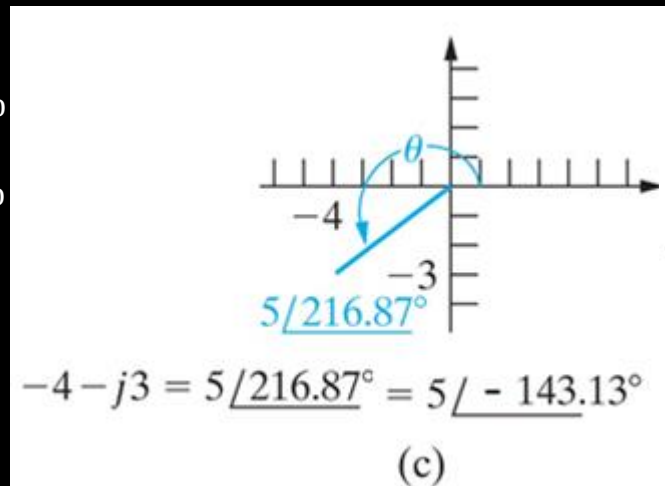

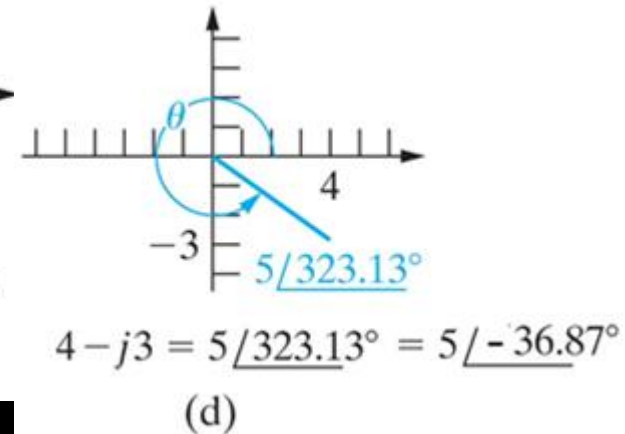
$$-143.13^\circ = -180^\circ + 36.87^\circ$$


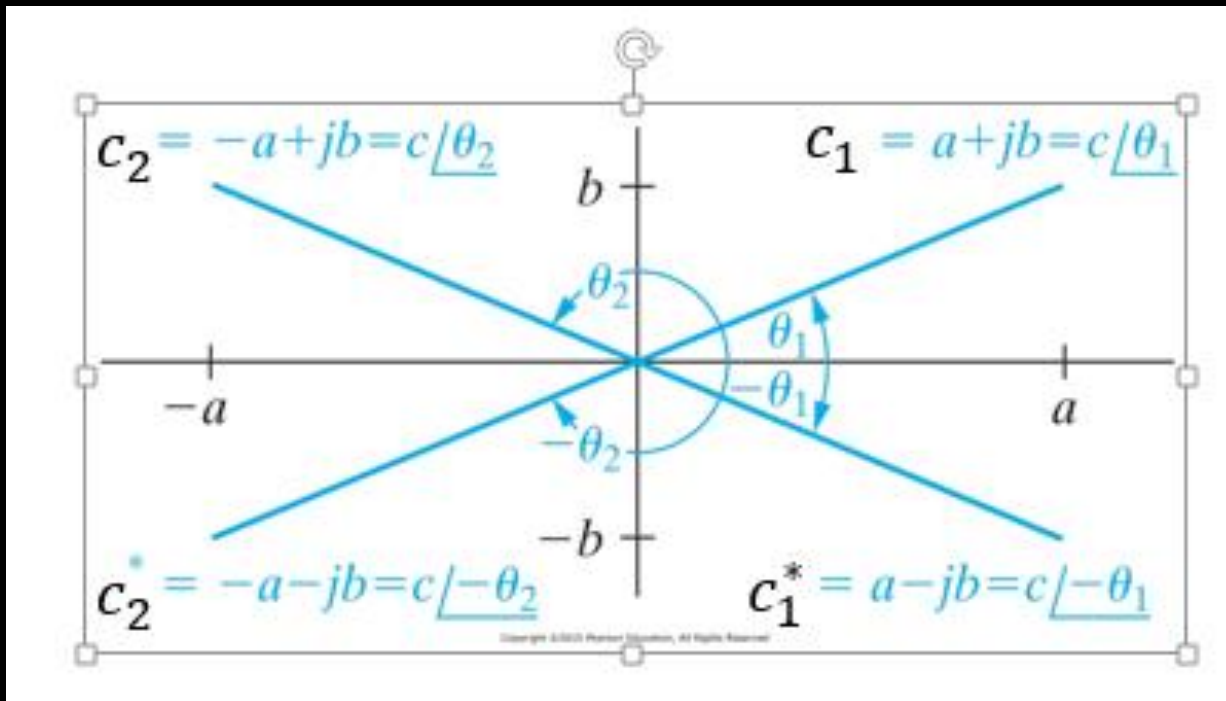
# Conjugate Complex Numbers

If  $c_1 = a + jb$ ,  $c = a - jb$ ,  $c_1$  and  $c$  are called conjugate numbers, denoted by  $c = c_1^*$



# Complex Numbers Operations

## Addition/Subtraction

If we have two complex numbers

$$c_1 = a_1 + jb_1$$

$$c_2 = a_2 + jb_2$$

$$\begin{aligned}\text{Then } c = c_1 \pm c_2 &= (a_1 + jb_1) \pm (a_2 + jb_2) \\ &= (a_1 \pm a_2) + j(b_1 \pm b_2)\end{aligned}$$

For example:  $c_1 = 8 + j16, c_2 = 12 - j3$

$$c_1 + c_2 = (8 + 12) + j(16 - 3) = 20 + j13$$

$$c_1 - c_2 = (8 - 12) + j(16 + 3) = -4 + j19$$

# Complex Number Operations

## Multiplication/Division

If we have two complex numbers

$$c_1 = a_1 + jb_1 = r_1 e^{j\theta_1}$$

$$c_2 = a_2 + jb_2 = r_2 e^{j\theta_2}$$

$$c_1 c_2 = (r_1 e^{j\theta_1})(r_2 e^{j\theta_2}) = r_1 r_2 e^{j(\theta_1 + \theta_2)}$$

$$\frac{c_1}{c_2} = \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}} = \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)}$$

For example:  $c_1 = 4 + j3 = 5e^{j36.87^\circ}$ ,  $c_2 = 4 - j3 = 5e^{-j36.87^\circ}$

$$c_1 c_2 = 5 \times 5 e^{j[36.87^\circ + (-36.87^\circ)]} = 25$$

$$\frac{c_1}{c_2} = \frac{5}{5} e^{j36.87^\circ - (-36.87^\circ)} = e^{j73.74^\circ}$$

# Useful Identities

$$j = \sqrt{-1}$$

$$j^2 = -1$$

$$(-j)j = 1$$

$$j = \frac{1}{-j}$$

$$e^{\pm j\pi} = \cos(\pi) \pm j\sin(\pi) = -1$$

$$e^{\pm j\frac{\pi}{2}} = \cos\left(\frac{\pi}{2}\right) \pm j\sin\left(\frac{\pi}{2}\right) = \pm j$$

$$a^2 - b^2 = (a + b)(a - b)$$

$$a^2 + b^2 = a^2 - (jb)^2 = (a + jb)(a - jb)$$



# The Inverse Laplace Transform

An integral inverse Laplace transform is defined as:

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = \frac{1}{2\pi j} \lim_{T \rightarrow \infty} \int_{\gamma - jT}^{\gamma + jT} F(s) e^{st} ds$$

where the integration is performed along the vertical line  $\text{Re}(s) = \gamma$  in the complex plane such that  $\gamma$  is greater than the real part of all roots of  $F(s)$ .

# Rational Functions

The general form of Laplace transform of a function is:

$$F(s) = \frac{N(s)}{D(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}$$

where the coefficient  $a$  and  $b$  are real constant, and the exponents  $m$  and  $n$  are natural numbers.

If  $m > n$ ,  $\frac{N(s)}{D(s)}$  is called a **proper rational function**;

If  $m \leq n$ ,  $\frac{N(s)}{D(s)}$  is called an **improper rational function**.

# Partial Fraction Expansion

A *proper rational function* can be expanded into a sum of partial fraction by writing a term or a series terms for each root of  $D(s)$ .

$$\begin{aligned} F(s) &= \frac{N(s)}{D(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0} \\ &= \frac{K(a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0)}{(s + p_1)(s + p_2) \dots (s + p_m)} \quad m > n \end{aligned}$$

The roots of  $D(s)$  might be

1. distinct and real
2. distinct and complex
3. repeated and real
4. repeated and complex

# Improper Rational Functions

- ▶ *Improper rational functions cannot be expanded into partial fractions.* However, you can convert an improper rational function into a polynomial + a proper rational function by using a long division method.

For example  $F(s) = \frac{s^2+s+1}{s+1} = s + \frac{1}{s+1}$

Polynomial function of  $s$

Proper rational function of  $s$

And we know:  $\mathcal{L}\{\delta'(t)\} = s$ , (Problem 12.12)  $\mathcal{L}\{\delta^{(n)}(t)\} = s^n$  (Problem 12.11)

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = \delta'(t) + e^{-t}, \quad t > 0$$

# The Inverse Laplace Transform

1.  $D(s)$  has distinct real roots, and  $l < q$

$$\begin{aligned} F(s) &= \frac{N(s)}{D(s)} = \frac{a_l s^l + a_{l-1} s^{l-1} + \cdots + a_1 s + a_0}{b_q s^q + b_{q-1} s^{q-1} + \cdots + b_1 s + b_0} \\ &= \frac{K(a_l s^l + a_{l-1} s^{l-1} + \cdots + a_1 s + a_0)}{(s + p_1)(s + p_2) \cdots (s + p_q)} \\ &\equiv \frac{k_1}{s + p_1} + \frac{k_2}{s + p_2} + \frac{k_3}{s + p_3} + \cdots + \frac{k_q}{s + p_q} \end{aligned}$$

where  $-p_i, i = 1, 2, 3, \dots, q$ , are real and distinct.

$$\begin{aligned} k_i &= F(s)(s + p_i)|_{s=-p_i} \\ f(t) &= \mathcal{L}^{-1}\left\{\frac{k_1}{s + p_1} + \frac{k_2}{s + p_2} + \frac{k_3}{s + p_3} + \cdots + \frac{k_q}{s + p_q}\right\} \\ &= (k_1 e^{-p_1 t} + k_2 e^{-p_2 t} + k_3 e^{-p_3 t} + \cdots + k_q e^{-p_q t})u(t) \end{aligned}$$

# The Inverse Transform-Example

$$F(s) = \frac{96(s+5)(s+12)}{s(s+8)(s+6)} \equiv \frac{k_1}{s} + \frac{k_2}{s+8} + \frac{k_3}{s+6}$$

Both sides are multiplied by  $s$  and then evaluated at  $s=0$ :

$$\left. \frac{96(s+5)(s+12)s}{s(s+8)(s+6)} \right|_{s=0} \equiv k_1 + \left. \frac{k_2 s}{s+8} \right|_{s=0} + \left. \frac{k_3 s}{s+6} \right|_{s=0}$$

$$k_1 = \left. \frac{96(s+5)(s+12)s}{s(s+8)(s+6)} \right|_{s=0} = F(s)s \Big|_{s=0} = \frac{96(5)(12)}{(8)(6)} = 120$$

Similarly,


$$k_2 = \left. \frac{96(s+5)(s+12)}{s(s+6)} \right|_{s=-8} = F(s)(s+8) \Big|_{s=-8} = \frac{96(-3)(4)}{(-8)(-2)} = -72$$

$$k_3 = \left. \frac{96(s+5)(s+12)}{s(s+8)} \right|_{s=-6} = F(s)(s+6) \Big|_{s=-6} = \frac{96(-1)(6)}{(-6)(2)} = 48$$


$$F(s) = \frac{96(s+5)(s+12)}{s(s+8)(s+6)} \equiv \frac{120}{s} + \frac{-72}{s+8} + \frac{48}{s+6}$$

$$f(t) = (120 - 72e^{-8t} + 48e^{-6t})u(t)$$
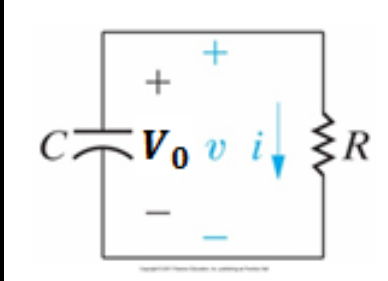
# Applications of the Laplace Transform – The First Order RC Circuit



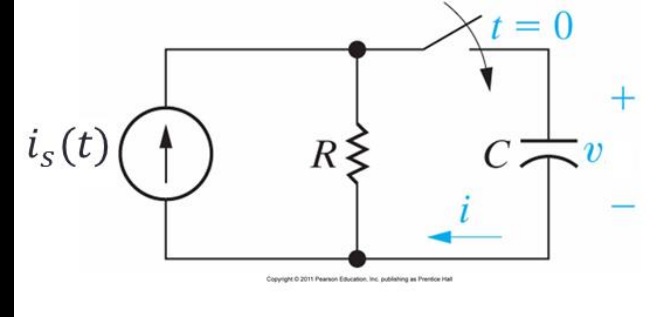Apply Laplace transform to the both sides of the equation




$$C \frac{dv(t)}{dt} + \frac{v(t)}{R} = 0 \Rightarrow V(s) = \frac{V_0}{s + \frac{1}{RC}}$$

$$C \frac{dv(t)}{dt} + \frac{v(t)}{R} = i_s(t) \text{ and } i_s(t) = I_s$$


The natural response is:  $v(t) = \mathcal{L}^{-1}\{V(s)\} = V_0 e^{-\frac{1}{RC}t}$
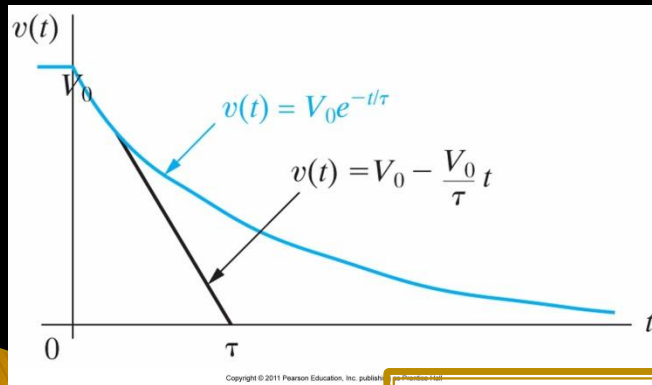
$$V(s) = \frac{\frac{1}{C} I_s}{s(s + \frac{1}{RC})}$$




The step response is:
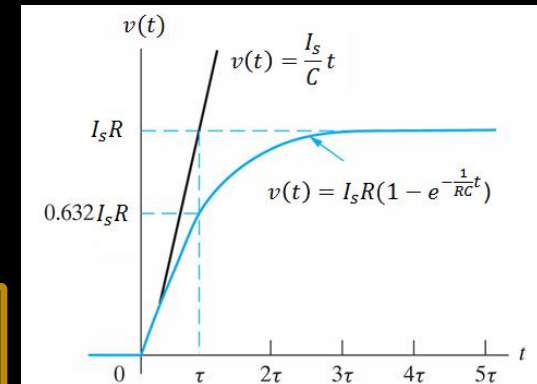
$$v(t) = I_s R (1 - e^{-\frac{1}{RC}t})$$




The time constant of RC circuits is:  $\tau = RC$
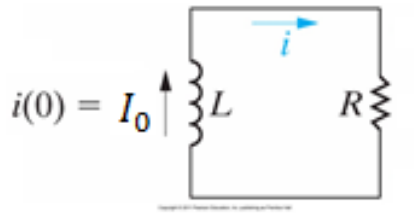
# Applications of the Laplace Transform– The First Order RL Circuit



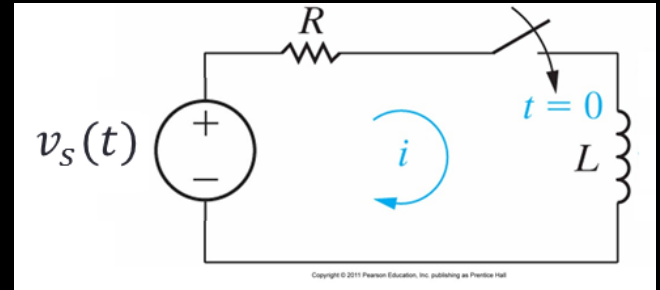Apply Laplace transform to the both sides of the equation



$$L \frac{di(t)}{dt} + Ri(t) = 0 \Rightarrow I(s) = \frac{I_0}{s + R/L}$$

$$L \frac{di(t)}{dt} + Ri(t) = v_s(t) \text{ and } v_s(t) = V_s$$


The natural response is:

$$i(t) = \mathcal{L}^{-1}\{I(s)\} = I_0 e^{-\frac{R}{L}t}$$


$$I(s) = \frac{V_s/L}{s(s + \frac{R}{L})}$$

The step response is:
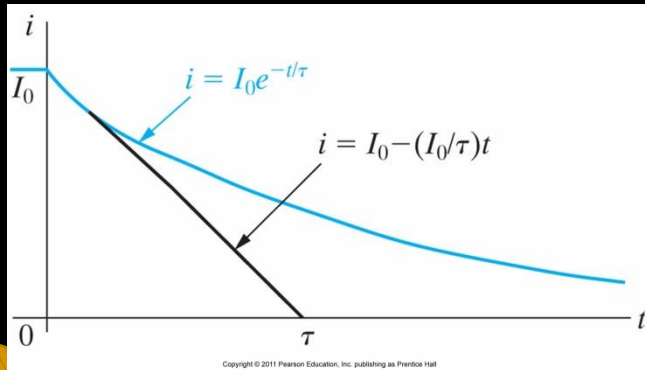
$$i(t) = \frac{V_s}{R} (1 - e^{-\frac{R}{L}t})$$



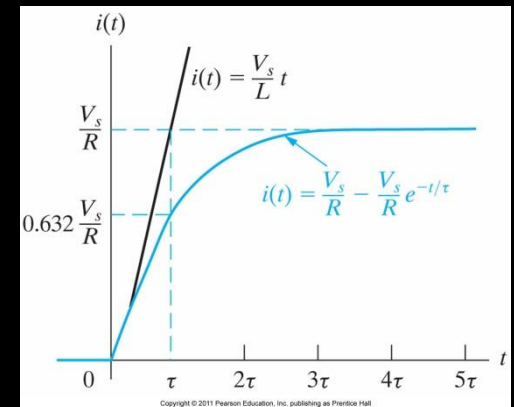The time constant of RL circuits is  $\tau = \frac{L}{R}$





# The Inverse Transform

2.  $D(s)$  has distinct complex roots and  $l < q$

$$\begin{aligned} F(s) &= \frac{N(s)}{D(s)} = \frac{a_l s^l + a_{l-1} s^{l-1} + \dots + a_1 s + a_0}{b_q s^q + b_{q-1} s^{q-1} + \dots + b_1 s + b_0} \\ &= \frac{K(a_l s^l + a_{l-1} s^{l-1} + \dots + a_1 s + a_0)}{(s + p_1)(s + p_2) \dots (s + p_q)} \equiv \frac{k_1}{s + p_1} + \frac{k_2}{s + p_2} + \frac{k_3}{s + p_3} + \dots + \frac{k_q}{s + p_q} \end{aligned}$$

where  $-p_i, i = 1, 2, 3, \dots, q$ , are complex and distinct.

$$k_i = F(s)(s + p_i)|_{s=-p_i}$$

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = (k_1 e^{-p_1 t} + k_2 e^{-p_2 t} + k_3 e^{-p_3 t} + \dots + k_q e^{-p_q t})u(t)$$

- Note: In realizable circuits, complex roots always appear in conjugate pair and their corresponding coefficients are themselves complex conjugate.

# The Inverse Transform–Example

$$\begin{aligned} F(s) &= \frac{100(s+3)}{(s+6)(s^2+6s+25)} = \frac{100(s+3)}{(s+6)(s+3-j4)(s+3+j4)} \\ &\equiv \frac{k_1}{s+6} + \frac{k_2}{s+3-j4} + \frac{k_3}{s+3+j4} \end{aligned}$$

$$k_1 = F(s)(s+6) \Big|_{s=-6} = \frac{100(s+3)}{(s^2+6s+25)} \Big|_{s=-6} = \frac{100(-3)}{36+6(-6)+25} = -12$$

$$\begin{aligned} k_2 &= F(s)(s+3-j4) \Big|_{s=-3+j4} = \frac{100(s+3)}{(s+6)(s+3+j4)} \Big|_{s=-3+j4} = \frac{100(j4)}{(3+j4)(j8)} \\ &= 6 - j8 = 10e^{-j53.13^\circ} \end{aligned}$$

$$\begin{aligned} k_3 &= F(s)(s+3+j4) \Big|_{s=-3-j4} = \frac{100(s+3)}{(s+6)(s+3-j4)} \Big|_{s=-3-j4} = \frac{100(-j4)}{(3-j4)(-j8)} \\ &= 6 + j8 = 10e^{j53.13^\circ} \end{aligned}$$

**$k_2$  and  $k_3$  are complex conjugate. So  $k_3 = k_2^*$**

# The Inverse Transform–Example

$$F(s) = \frac{100(s+3)}{(s+6)(s^2+6s+25)} \equiv \frac{-12}{s+6} + \frac{10e^{-j53.13^\circ}}{s+3-j4} + \frac{10e^{j53.13^\circ}}{s+3+j4}$$

$$\begin{aligned} f(t) &= \left[ -12e^{-6t} + 10e^{-j53.13^\circ} e^{-(3-j4)t} + 10e^{j53.13^\circ} e^{-(3+j4)t} \right] u(t) \\ &= \left[ -12e^{-6t} + 10 \times e^{-3t} \left( 2 \times \frac{e^{j(4t-53.13^\circ)} + e^{-j(4t-53.13^\circ)}}{2} \right) \right] u(t) \\ &= [-12e^{-6t} + 20e^{-3t} \cos(4t - 53.13^\circ)] u(t) \end{aligned}$$

In general:

$$\mathcal{L}^{-1} \left\{ \frac{K}{s + \alpha - j\beta} + \frac{K^*}{s + \alpha + j\beta} \right\} = 2|K|e^{-\alpha t} \cos(\beta t + \theta)$$

Where  $K = |K|e^{j\theta}$  and  $K^* = |K|e^{-j\theta}$ .

# The Inverse Transform

3.  $D(s)$  has repeated real roots and  $l < q$

$$\begin{aligned} F(s) &= \frac{N(s)}{D(s)} = \frac{a_l s^l + a_{l-1} s^{l-1} + \dots + a_1 s + a_0}{b_q s^q + b_{q-1} s^{q-1} + \dots + b_1 s + b_0} \\ &= \frac{K(a_l s^l + a_{l-1} s^{l-1} + \dots + a_1 s + a_0)}{(s + p)^q} \\ &\equiv \frac{k_1}{(s + p)^q} + \frac{k_2}{(s + p)^{q-1}} + \frac{k_3}{(s + p)^{q-2}} + \dots + \frac{k_q}{s + p} \end{aligned}$$

where  $-p$  is a real root of multiplicity  $q$ .

$$k_i = \frac{1}{(i-1)!} \frac{d^{(i-1)}}{ds^{(i-1)}} [F(s)(s+p)^q] \Big|_{s=-p}$$

$$\begin{aligned} f(t) &= \mathcal{L}^{-1}\{F(s)\} \\ &= [k_1 \frac{t^{q-1}}{(q-1)!} e^{-pt} + k_2 \frac{t^{q-2}}{(q-2)!} e^{-pt} + k_3 \frac{t^{q-3}}{(q-3)!} e^{-pt} + \dots + k_q e^{-pt}] u(t) \end{aligned}$$

# The Inverse Transform-Example

$$F(s) = \frac{100(s+25)}{s(s+5)^3} \equiv \frac{k_4}{s} + \frac{k_1}{(s+5)^3} + \frac{k_2}{(s+5)^2} + \frac{k_3}{s+5}$$

$$k_4 = F(s)s \Big|_{s=0} = \frac{100(s+25)}{(s+5)^3} \Big|_{s=0} = \frac{100(25)}{125} = 20$$

$$k_1 = F(s)(s+5)^3 \Big|_{s=-5} = \frac{100(s+25)}{s} \Big|_{s=-5} = \frac{100(20)}{-5} = -400$$

$$k_2 = \frac{d[F(s)(s+5)^3]}{ds} \Big|_{s=-5} = \frac{d}{ds} \left[ \frac{100(s+25)}{s} \right] \Big|_{s=-5} = 100 \left[ \frac{s - (s+25)}{s^2} \right] \Big|_{s=-5} = -100$$

$$k_3 = \frac{1}{2} \frac{d^2[F(s)(s+5)^3]}{ds^2} \Big|_{s=-5} = \frac{1}{2} \frac{d^2}{ds^2} \left[ \frac{100(s+25)}{s} \right] \Big|_{s=-5} = 50 \left( \frac{50}{s^3} \right) \Big|_{s=-5} = -20$$

$$F(s) = \frac{20}{s} - \frac{400}{(s+5)^3} - \frac{100}{(s+5)^2} - \frac{20}{s+5}$$

$$f(t) = (20 - 200t^2e^{-5t} - 100te^{-5t} - 20e^{-5t})u(t)$$

# Applications in Series-connected RLC Circuits

At  $t = 0$ , the switch is closed and  $i(0^-) = 0$ ,  $v(0^-) = 0$ .

$$Ri(t) + L \frac{d}{dt} i(t) + v(t) = v_s(t)$$

$$i(t) = C \frac{d}{dt} v(t)$$


Applying Laplace transform to the both sides of the above equations and assuming  $V(s) = \mathcal{L}\{v(t)\}$ ,  $V_s(s) = \mathcal{L}\{v_s(t)\}$ , we have:

$$RI(s) + sLI(s) + V(s) = V_s(s)$$

$$I(s) = sCV(s)$$


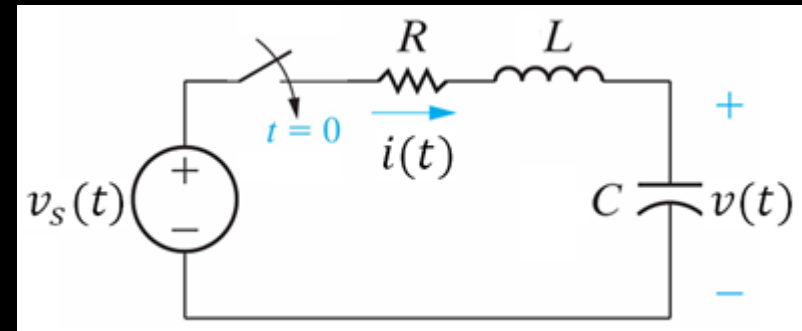
$$V(s) = \frac{V_s(s)/LC}{s^2 + \left(\frac{R}{L}\right)s + (1/LC)}$$



From  $D(s) = s^2 + \left(\frac{R}{L}\right)s + \left(\frac{1}{LC}\right) = 0$ , we have

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where  $\alpha = \frac{R}{2L}$  : **neper frequency**

$\omega_0 = \frac{1}{\sqrt{LC}}$  : **resonant radian frequency**

# Applications in Series-connected RLC Circuits

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} .$$

Let's assume  $v_s(t) = V_f$ ; a DC source


1. If  $\alpha > \omega_0$ ,  $s_1$  and  $s_2$  are real and distinct, the voltage response is called **overdamped**.  
$$v(t) = V_f + k_1 e^{s_1 t} + k_2 e^{s_2 t}$$
2. If  $\alpha < \omega_0$ ,  $s_1$  and  $s_2$  are distinct and complex, the voltage response is called **underdamped**.

$$v(t) = V_f + k_1 e^{-\alpha t} \cos(\omega_d t) + k_2 e^{-\alpha t} \sin(\omega_d t) = V_f + k e^{-\alpha t} \cos(\omega_d t + \theta)$$

where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ , which is called **damped radian frequency**.

3. If  $\alpha = \omega_0$ ,  $s_1$  and  $s_2$  are repeated real roots, the response is called **critically damped**.  
$$v(t) = V_f + k_1 t e^{-\alpha t} + k_2 e^{-\alpha t}$$

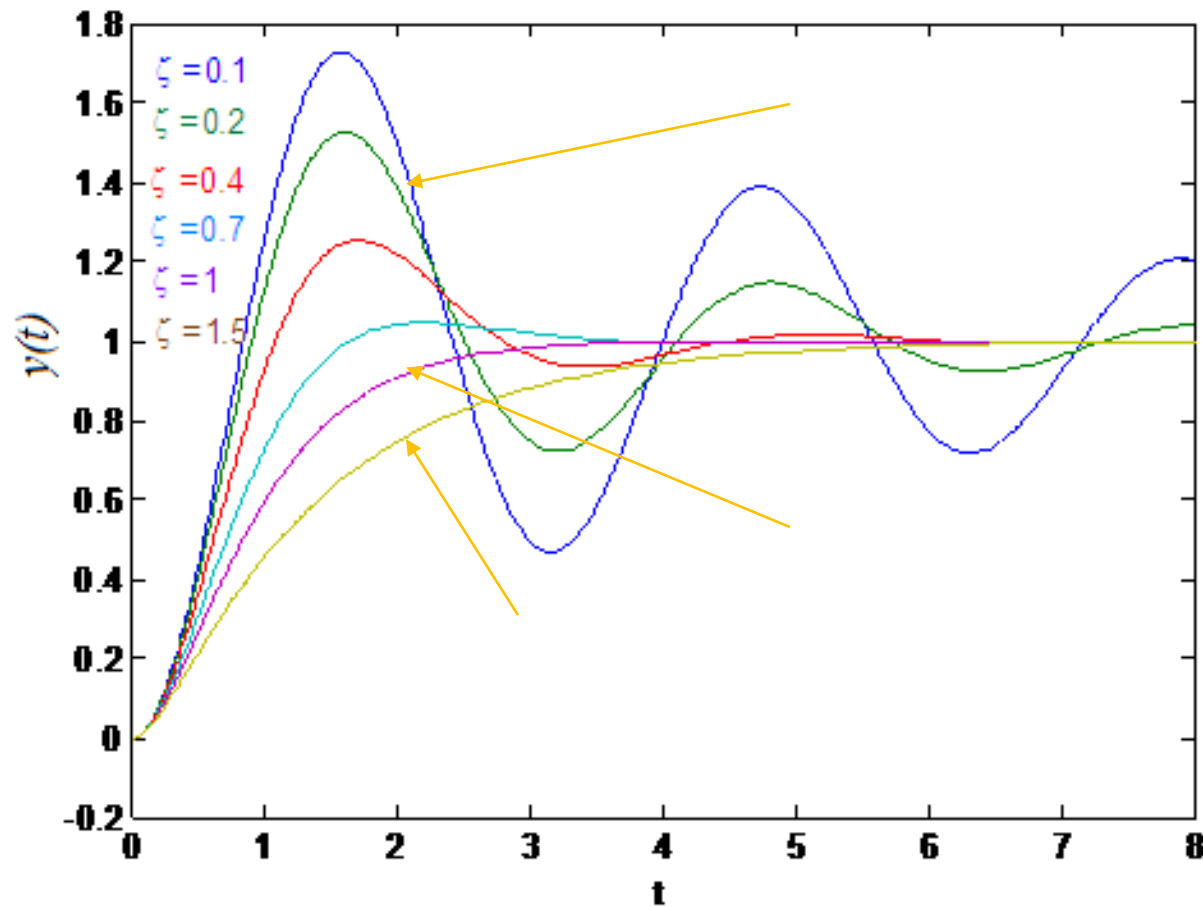
# Applications in Series-connected RLC Circuits



$\zeta = \frac{\alpha}{\omega_0}$  is called damping ratio.


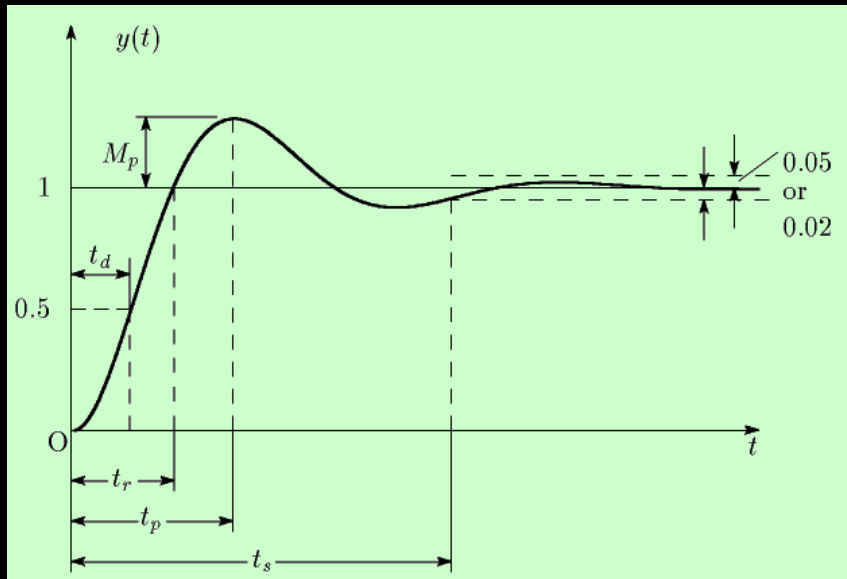
# Applications in Series-connected RLC Circuits



$t_p$ : Peak time(required for the response to reach the first peak value).

$t_s$ : Settling time(required for the response to reach and stay with 2% or 5% final value).



$M_p$ : Maximum percent overshoot

$$M_p = \frac{y(t_p) - y(\infty)}{y(\infty)}$$

$t_d$ : Delay time(required for the response to reach half of the final the very first time).

$t_r$ : Rise time(required for the response to rise from 0 to100% of the final value. (For the overdamped or critically damped circuit, the rise time from 10% to 90% is commonly used).
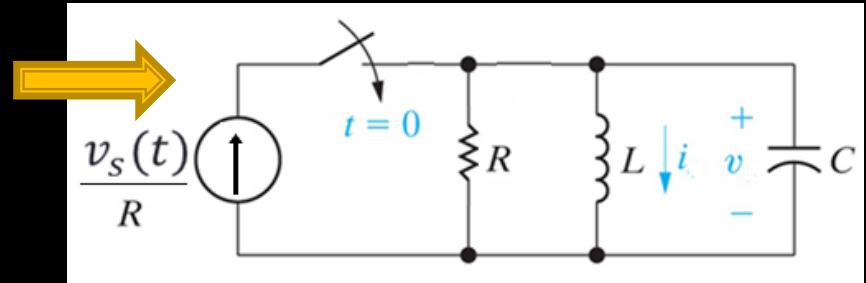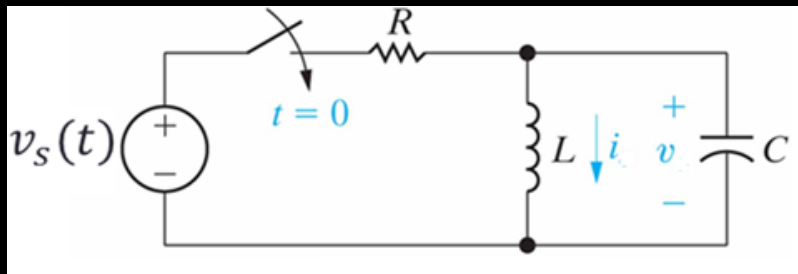
# Applications in Parallel-connected RLC Circuits



At  $t = 0$ , the switch is closed and  $i(0^-) = 0$ ,  $v(0^-) = 0$ . Applying KCL to the above circuit, we have:

$$\frac{v(t)}{R} + \frac{1}{L} \int_{0^-}^t v(x) dx + C \frac{d}{dt} v(t) = \frac{v_s(t)}{R}$$

Applying Laplace transform to both sides of the above equations and assuming  $V(s) = \mathcal{L}\{v(t)\}$ ,  $V_s(s) = \mathcal{L}\{v_s(t)\}$ , we have:

$$V(s) = \frac{sV_s(s)/RC}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)}$$

$$I(s) = \frac{V_s(s)/RLC}{s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right)}$$

From  $D(s) = s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right) = 0$ , we have:

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where  $\alpha = \frac{1}{2RC}$  : **neper frequency**

$\omega_0 = \frac{1}{\sqrt{LC}}$  : **resonant radian frequency**


# Applications in Parallel-connected RLC Circuits

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}.$$

Let's assume  $v_s(t) = V_f$ ; A DC source

1. If  $\alpha > \omega_0$ ,  $s_1$  and  $s_2$  are real and distinct, the voltage response is called **overdamped**.  
$$v(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$
2. If  $\alpha < \omega_0$ ,  $s_1$  and  $s_2$  are distinct and complex, the voltage response is called **underdamped**.  
$$v(t) = k_1 e^{-\alpha t} \cos(\omega_d t) + k_2 e^{-\alpha t} \sin(\omega_d t) = k e^{-\alpha t} \cos(\omega_d t + \theta)$$
  
where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ , which is called **damped radian frequency**.
3. If  $\alpha = \omega_0$ ,  $s_1$  and  $s_2$  are repeated real roots, the response is called **critically damped**.  
$$v(t) = k_1 t e^{-\alpha t} + k_2 e^{-\alpha t}$$
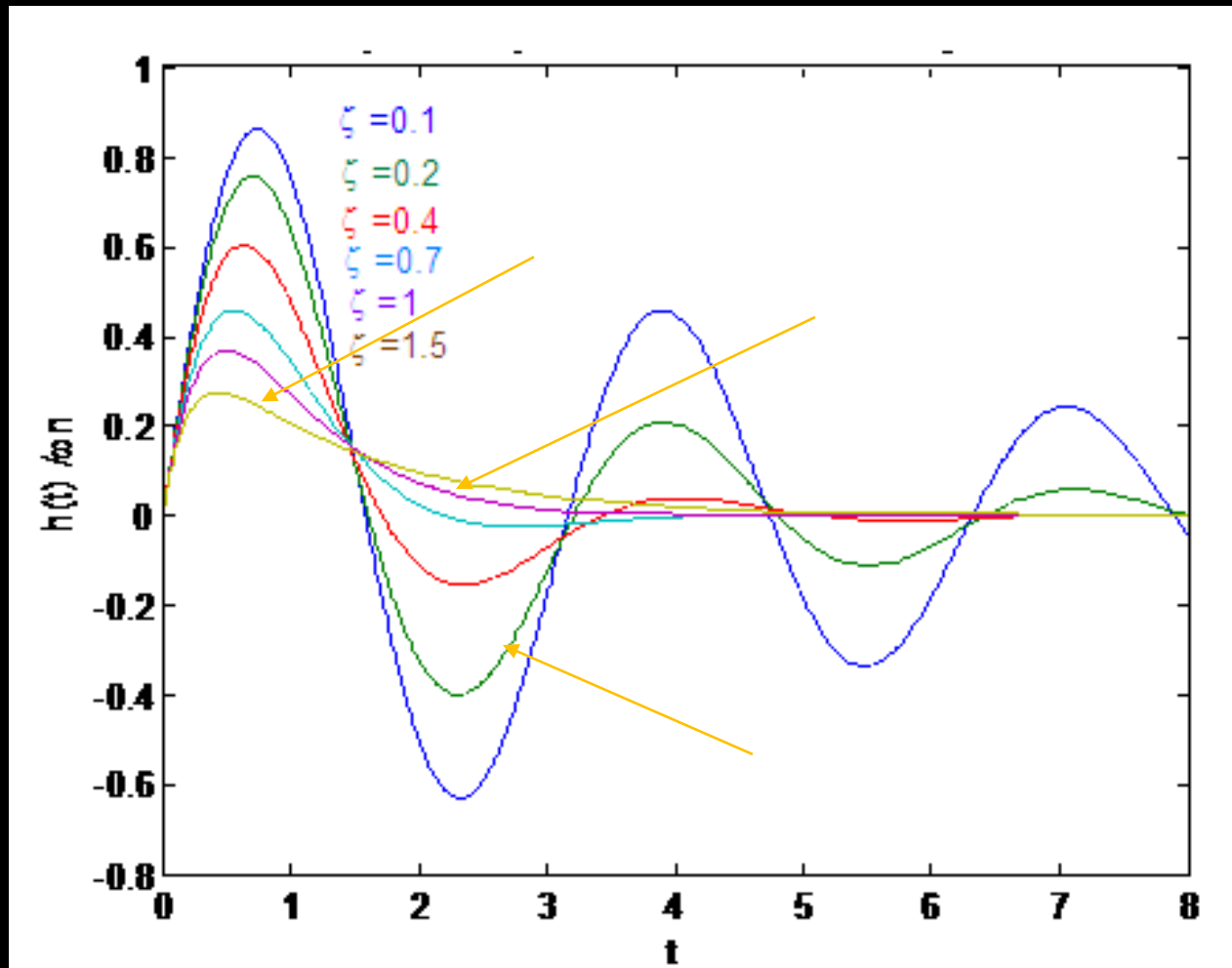
# Applications in Parallel-connected RLC Circuits



# The Inverse Transform

4.  $D(s)$  has Repeated complex roots *and*  $l < 2q$

$$F(s) = \frac{N(s)}{D(s)} = \frac{K(a_l s^l + a_{l-1} s^{l-1} + \dots + a_1 s + a_0)}{(s + p)^q (s + \bar{p})^q} \equiv \frac{k_1}{(s + p)^q} + \frac{k_1'}{(s + \bar{p})^q} + \dots + \frac{k_q}{s + p} + \frac{k_q'}{s + \bar{p}}$$

$$k_i = \frac{1}{(i-1)!} \frac{d^{(i-1)}}{ds^{(i-1)}} [F(s)(s + p)^q] \Big|_{s=-p}, \quad k_i' = \frac{1}{(i-1)!} \frac{d^{(i-1)}}{ds^{(i-1)}} [F(s)(s + \bar{p})^q] \Big|_{s=-\bar{p}}$$

where  $-p$  and  $-\bar{p}$  are a complex root of multiplicity  $q$ . They are conjugate.

$$f(t) = \mathcal{L}^{-1}\{F(s)\} = [k_1 \frac{t^{q-1}}{(q-1)!} e^{-pt} + k_1' \frac{t^{q-1}}{(q-1)!} e^{-\bar{p}t} + \dots + k_q e^{-pt} + k_q' e^{-\bar{p}t}] u(t)$$

Note: in realizable circuit, complex roots always appear in conjugate pair and their corresponding coefficients  $k_i$  and  $k_i'$  are themselves conjugate.

# The Inverse Transform

$$F(s) = \frac{768}{(s^2 + 6s + 25)^2} = \frac{768}{(s + 3 - j4)^2(s + 3 + j4)^2}$$
$$\equiv \frac{k_1}{(s + 3 - j4)^2} + \frac{k_2}{s + 3 - j4} + \frac{k_1^*}{(s + 3 + j4)^2} + \frac{k_2^*}{s + 3 + j4}$$

$$k_1 = F(s)(s + 3 - j4)^2 \Big|_{s=-3+j4} = \frac{768}{(s + 3 + j4)^2} \Big|_{s=-3+j4} = \frac{768}{(j8)^2} = -12$$

$$k_2 = \frac{d}{ds} F(s)(s + 3 - j4)^2 \Big|_{s=-3+j4} = -\frac{2(768)}{(s + 3 + j4)^3} \Big|_{s=-3+j4} = -\frac{1536}{(j8)^3}$$
$$= -j3 = 3e^{-j90^\circ}$$

$$F(s) \equiv \frac{-12}{(s + 3 - j4)^2} + \frac{3e^{-j90^\circ}}{s + 3 - j4} + \frac{-12}{(s + 3 + j4)^2} + \frac{3e^{j90^\circ}}{s + 3 + j4}$$

$$f(t) = [-24te^{-3t}\cos 4t + 6e^{-3t}\cos(4t - 90^\circ)]u(t).$$

# Summary

- If  $F(s)$  is a proper rational function, the inverse Laplace transform can be found by using a partial fraction expansion.
  - If  $F(s)$  is an improper rational function, it can be expanded as a polynomial function plus a proper rational function.
  - Four situations in the inverse Laplace transform were discussed based on the different types of roots of  $D(s)$ .
- 
- ▶ In next class, we will discuss
    - Poles and zeros
    - Initial- value and final-value theorems