





ENGR 065 Circuit Theory

Lecture 5: Simple Resistive Circuits

Today's Topics

- Series- and parallel-connected resistive circuits
 - How to simplify circuits using resistance combinations
 - Voltage and current divider circuits
-
- ❑ Covered in Section 3.1, 3.2, 3.3, and 3.4

Some Examples of Resistive Circuits

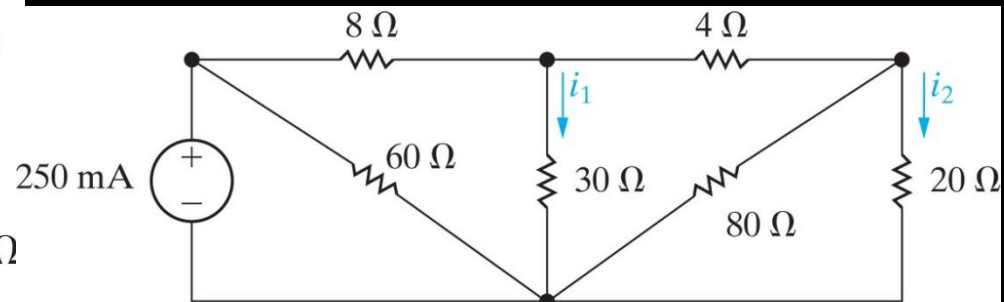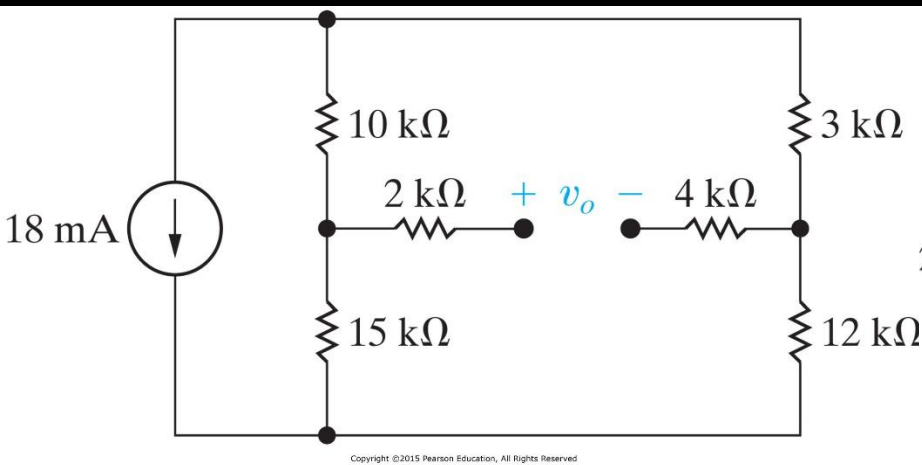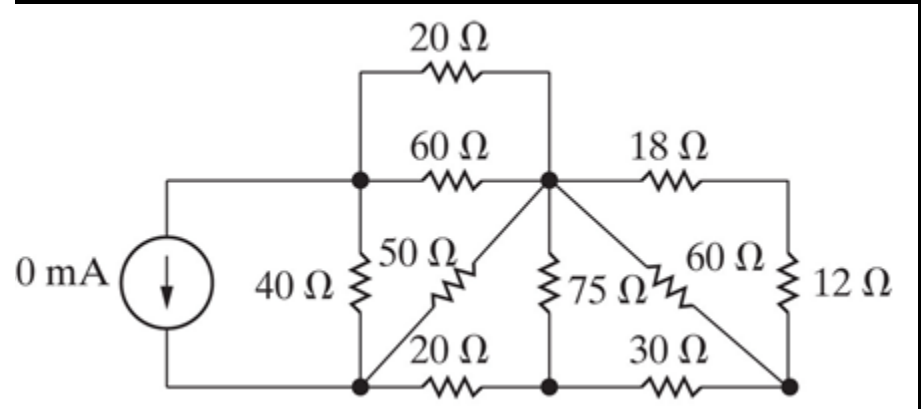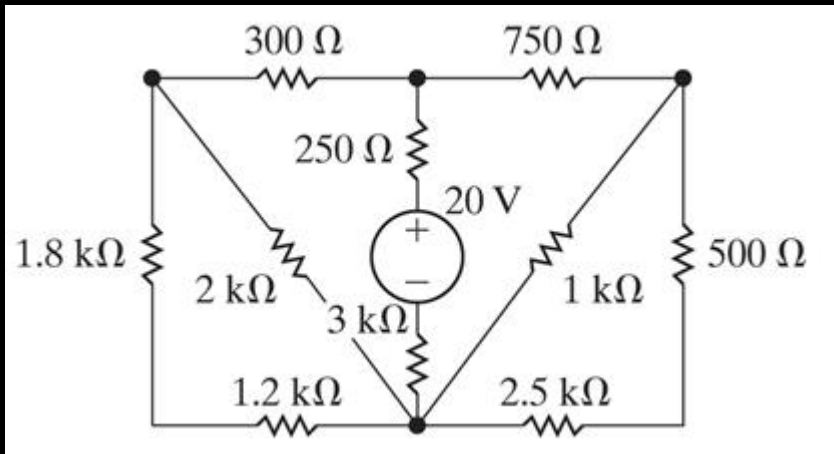

Copyright ©2015 Pearson Education, All Rights Reserved

Resistors in Series Connection

Resistors in series: two resistors connected **at a single node** and carry the **same current**.

Applying KVL to the circuit *on the right*:

$$v_s = v_1 + v_2 = iR_1 + iR_2 = i(R_1 + R_2)$$

So, the current in the circuit is:

$$i = \frac{v_s}{R_1 + R_2}$$



Assuming: $R_{eq} = R_1 + R_2$, then:

$$i = \frac{v_s}{R_{eq}}$$

R_{eq} is called equivalent resistance.

The solution can be extended to n series connected resistors:

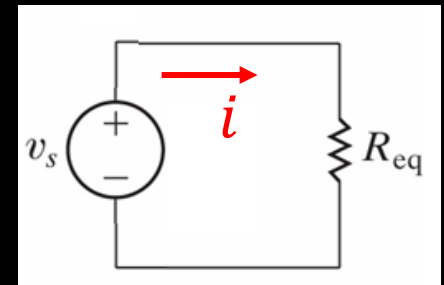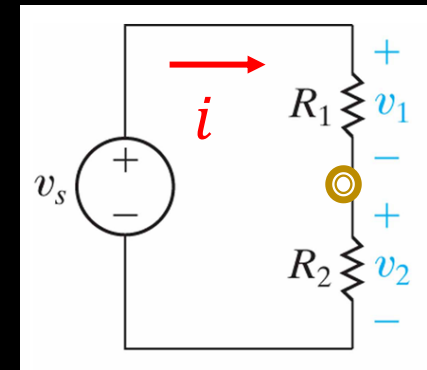
$$R_{eq} = R_1 + R_2 + \cdots + R_{n-1} + R_n \quad \text{so} \quad i = \frac{v_s}{R_{eq}}$$



Note that the equivalent resistance is always greater than the largest resistance of the resistor in the series connection.

Voltage-Divider Circuits

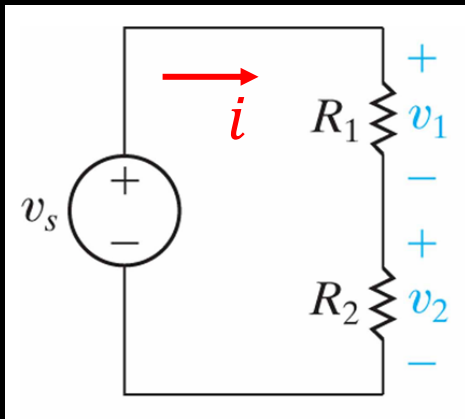A series connected resistive circuit can be used as a voltage divider. A voltage-divider circuit is used to develop **more than one voltage level** from **a single voltage source**.



$$i = \frac{v_s}{R_1 + R_2} \quad \text{Memorize me!}$$

$$v_1 = R_1 i = \frac{R_1 v_s}{R_1 + R_2} = \frac{R_1}{R_{eq}} v_s \quad \text{Memorize this!}$$


$$v_2 = R_2 i = \frac{R_2 v_s}{R_1 + R_2} = \frac{R_2}{R_{eq}} v_s \quad \text{Memorize this!}$$

If n resistors are series-connected, the voltage across the j th resistor is obtained by:

$$v_j = \frac{R_j}{R_{eq}} v_s$$


Resistors in Parallel Connection

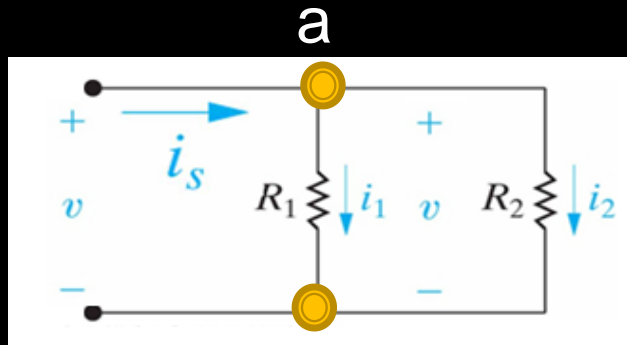When two resistors are connected at a node pair, they are in parallel. Parallel-connected resistors have the same voltage across their terminals.



Applying KCL at node a:
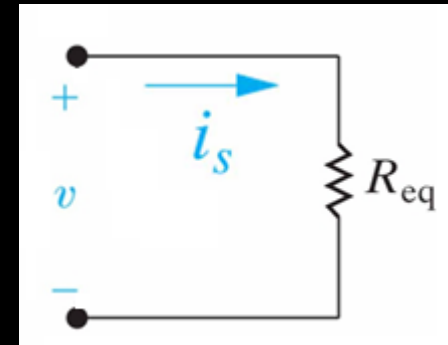
$$i_s = i_1 + i_2 = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$



Assuming $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$, we have:

$$i_s = v \frac{1}{R_{eq}}$$

$$v = R_{eq} i_s$$


R_{eq} is called equivalent resistance

If n resistors are parallel-connected, then $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_{n-1}} + \frac{1}{R_n}$

$$v = R_{eq} i_s$$


Note that the equivalent resistance is always **smaller than** the smallest resistance (not zero) of the resistor in the parallel connection.

Two Resistors in Parallel

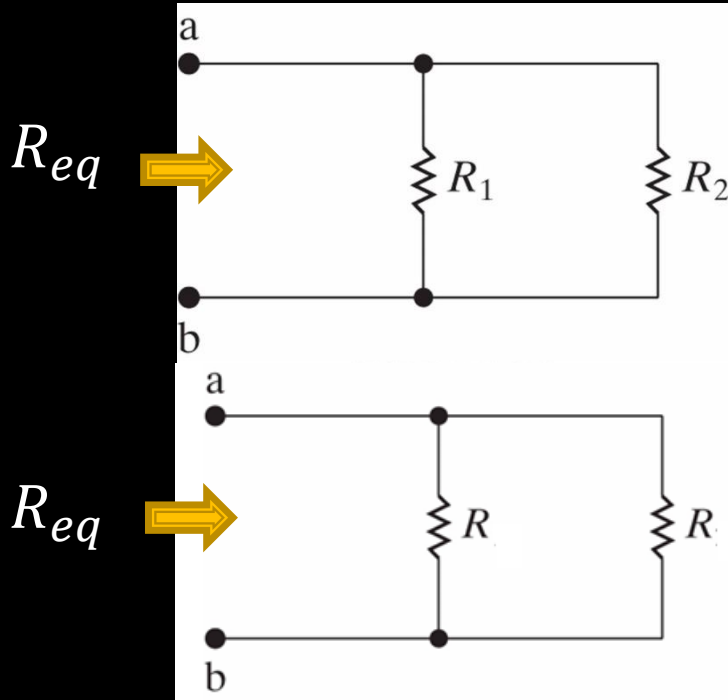


$$\text{From : } \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$
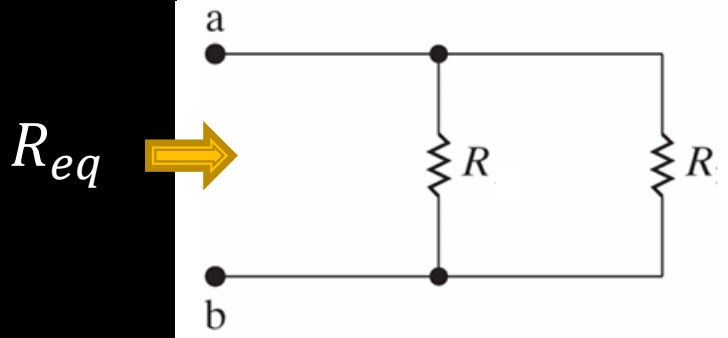
$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{Memorize this!}$$



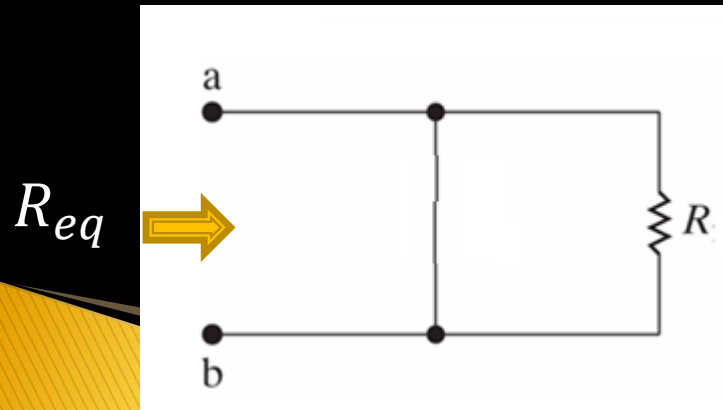
$$\text{If } R_1 = R_2 = R, R_{eq} = \frac{R}{2}$$



$$\text{If } R_1 = 0 \text{ or } R_2 = 0, R_{eq} = 0$$

Current-Divider Circuits

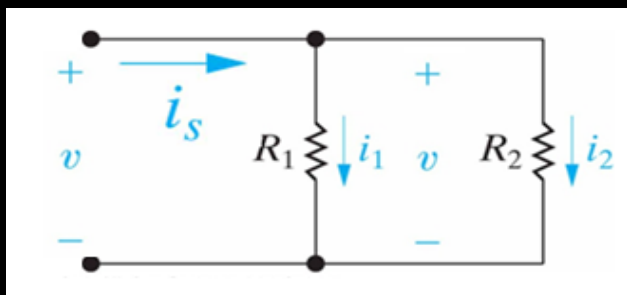A parallel connected resistive circuit can be used as a current-divider. The circuit is designed to divide **a current level** into **more than one current levels**.



$$\text{Where } R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

If n resistors are parallel-connected, the current in the j th resistor is obtained by:

$$i_j = \frac{R_{eq}}{R_j} i_s$$



$$v = R_{eq} i_s = \frac{R_1 R_2}{R_1 + R_2} i_s$$

Memorize these!

$$i_1 = \frac{v}{R_1} = \frac{R_{eq}}{R_1} i_s = \frac{R_2}{R_1 + R_2} i_s$$

$$i_2 = \frac{v}{R_2} = \frac{R_{eq}}{R_2} i_s = \frac{R_1}{R_1 + R_2} i_s$$

Example #1

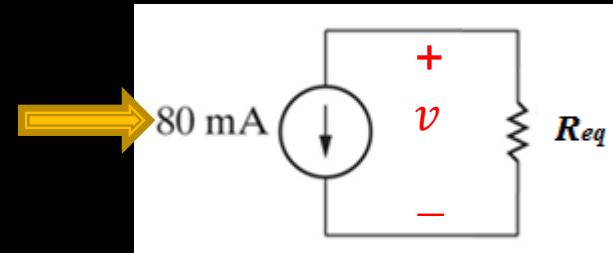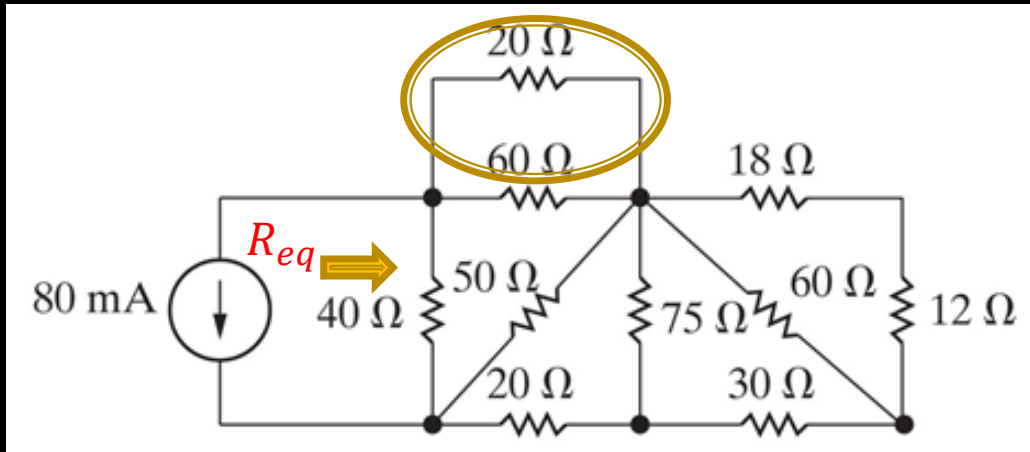

Find the power delivered by the source

$$18 + 12 = 30 \, \Omega$$

$$60 \parallel 30 = \frac{60 \times 30}{60 + 30} = 20 \, \Omega$$

$$20 + 30 = 50 \, \Omega$$

$$50 \parallel 75 = \frac{50 \times 75}{50 + 75} = 30 \, \Omega$$

$$30 + 20 = 50 \, \Omega$$

$$50 \parallel 50 = 25 \, \Omega$$

$$20 \parallel 60 = \frac{20 \times 60}{20 + 60} = 15 \, \Omega$$

$$25 + 15 = 40 \, \Omega$$


$$R_{eq} = 40 \parallel 40 = 20 \, \Omega$$

From Ohm's law: $v = -0.08 \times 20 = -1.6 \, V$

$$p_{80mA} = 0.08v = (0.08)(-1.6) = -128 \, mW$$

Or $p_{80mA} = -0.08^2 \times 20 = -128 \, mW < 0$
because the current source delivers power

Example #2

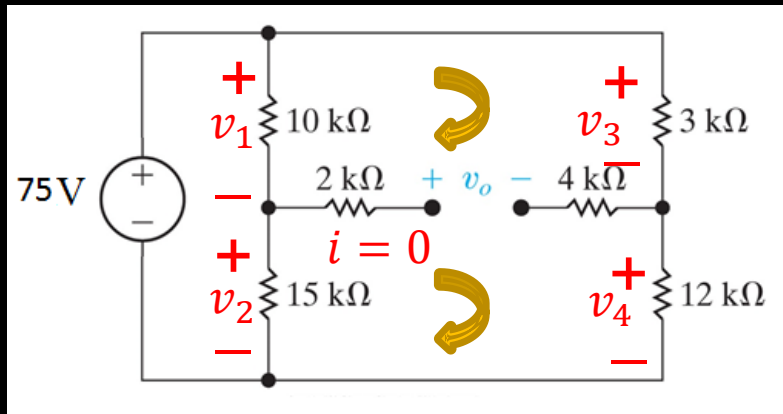

Find the voltage v_0 by using the voltage division or current division.

Applying KVL to the top loop: $v_3 - v_0 - v_1 = 0$ So $v_0 = v_3 - v_1$ (1)

Or applying KVL to the bottom loop: $v_4 - v_2 + v_0 = 0$ So $v_0 = v_2 - v_4$ (2)


Voltage division: $v_1 = \frac{10000 \times 75}{10000 + 15000} = 30 \text{ V}$ From KVL: $v_2 = 75 - 30 = 45 \text{ V}$

$v_3 = \frac{3000 \times 75}{3000 + 12000} = 15 \text{ V}$ From KVL: $v_4 = 75 - 15 = 60 \text{ V}$


From (1): $v_0 = v_3 - v_1 = 15 - 30 = -15 \text{ V}$

From (2): $v_0 = v_2 - v_4 = 45 - 60 = -15 \text{ V}$


Example #3

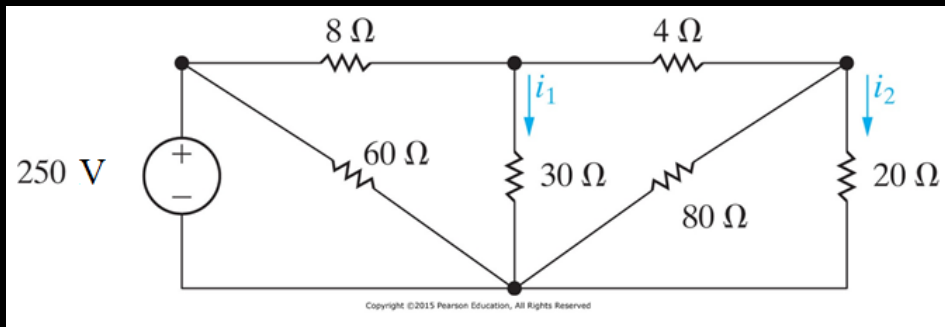

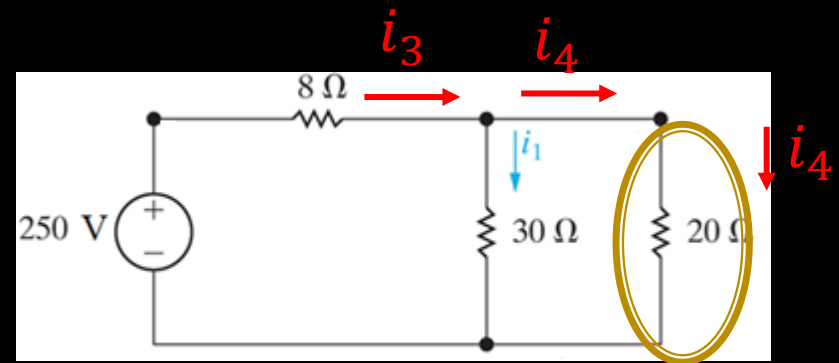Find i_1 and i_2 shown in the circuit above



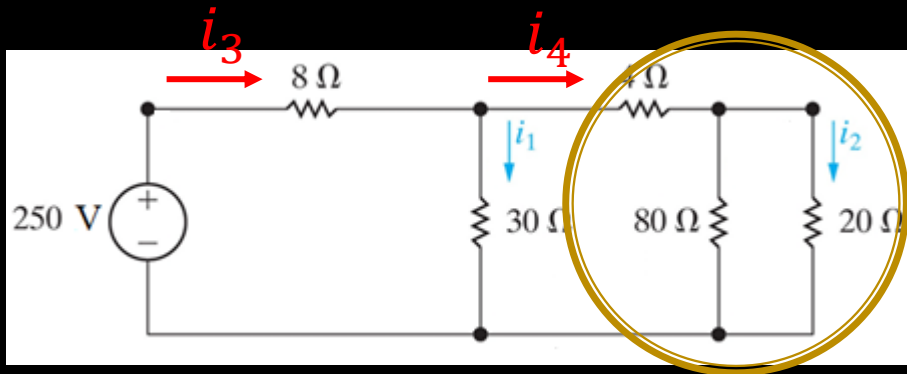
$$20 \parallel 30 = \frac{20 \times 30}{20 + 30} = 12 \Omega$$



$$20 \parallel 80 = \frac{20 \times 80}{20 + 80} = 16 \Omega$$

$$16 + 4 = 20 \Omega$$

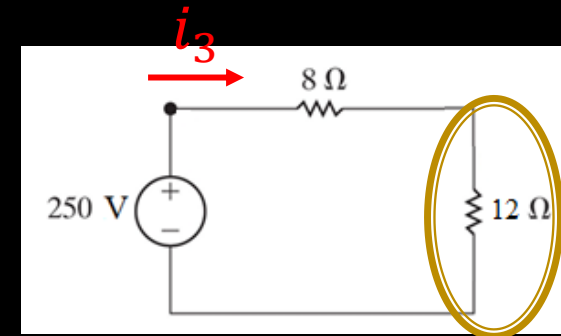

$$i_3 = \frac{250}{8 + 12} = 12.5 \text{ A}$$

$$i_1 = \frac{20 \times i_3}{30 + 20} = 5 \text{ A}$$

$$i_4 = \frac{30 \times i_3}{30 + 20} = 7.5 \text{ A}$$

$$i_2 = \frac{80 \times i_4}{80 + 20} = 6 \text{ A}$$

Summary

- ▶ Circuit simplification is one of the most important circuit analysis techniques.
- ▶ Two types of resistor connections: series and parallel connections.
- ▶ Series-connected resistive circuits can be used as the voltage dividers. Parallel-connected circuits can be used as the current dividers.

In next lecture, we will discuss:
The node-voltage method.