

Laboratory 8

Transient Responses of First Order RL and RC Circuits

(Round your calculation and simulation results to 2 decimal places if necessary)

Objectives


- Observe the transient responses of RL and RC circuits.
- Learn to how to measure time constant of first order circuits.

Equipment and components


- A computer
- PSPICE software

Preliminary

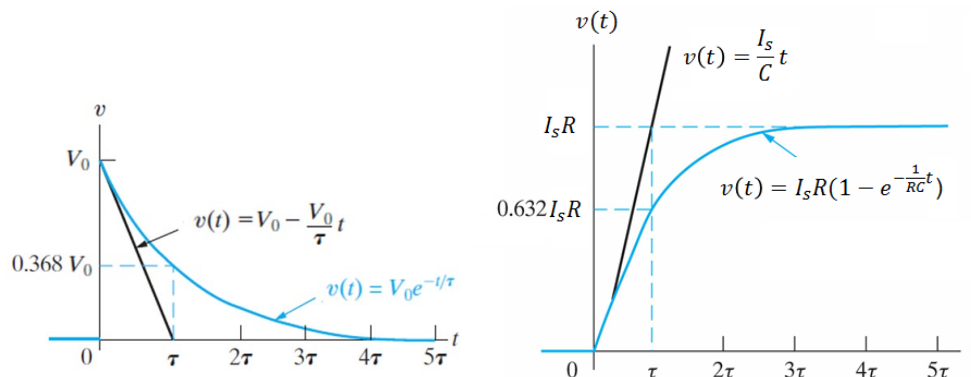- Read the lecture slides of “Inverse Laplace Transform and RC, RL, and RLC Circuits”.
- Calculate the time constant when $R = 1\text{ k}\Omega$, $C = 0.5\text{ }\mu\text{F}$, $C = 1\text{ }\mu\text{F}$, and $C = 2\text{ }\mu\text{F}$, respectively. Fill in Table 1. Refer to the natural and step responses of RC circuits shown below for finding the time constant.



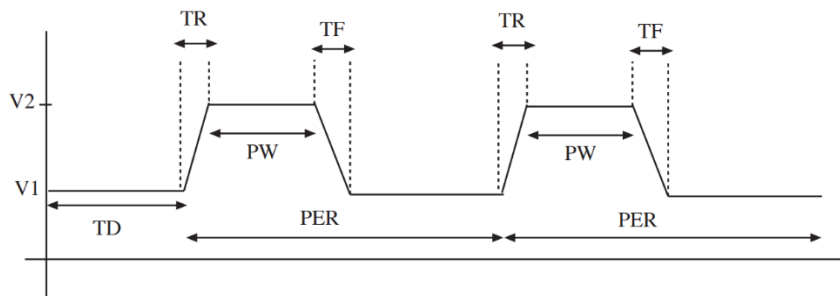
- Calculate the time constant when $R = 1\text{ }\Omega$, $L = 5\text{ mH}$, $L = 10\text{ mH}$, and $L = 20\text{ mH}$, respectively. Fill in Table 2. Refer to the above two graphs to find the time constant for the RL circuit.
- Pulse waveform: A voltage pulse source can be applied using VPULSE element in PSpice. VPULSE has 7 parameters that are described and shown below.



As an example, a square waveform can be created by setting $TR = TF = 0$ and $PER = 2 PW$. TD is the delay time.

Procedure

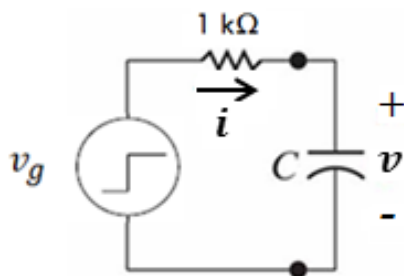1. Open PSpice and construct a circuit shown below with a resistor of $1\text{ k}\Omega$ and a capacitor of $1\mu\text{F}$. V_g is an independent voltage source generating square waveforms. Set $TR = TF = TD = 0$, $V_1 = 0$, $V_2 = 10\text{ V}$, and $PW = 4\text{ ms}$. Wisely set the period of the waveform so that you can clearly observe the natural and step responses $v(t)$ of the RC Circuit.



2. Measure $i(t)$ and $v(t)$. Plot them. What did you find? Why?
3. Fill the simulation results in Table 1

Table 1 Time Constant of RC Circuits

Resistance ($\text{k}\Omega$)	Capacitance (μF)	Calculated Time Constant	Measured Time Constant
1	0.5		
1	1		
1	2		


What did you find from the above table? Please explain.

4. let $R = 1\text{ k}\Omega$ and $TR = TF = TD = 0$, $V_1 = 0$, $V_2 = 10\text{ V}$, and $PER = 4\text{ ms}$, select the capacitance of the capacitor so that the response $v(t)$ of the circuit is a triangle waveform, as shown below.



What is your minimum value of the capacitance to generate the triangle waveform output?

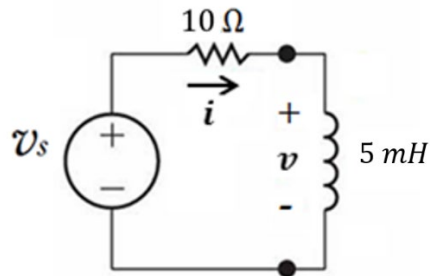5. Construct a circuit shown below with a resistor of $10\ \Omega$ and an inductor of 5 mH . Set $TR = TF = TD = 0$, $V_1 = 0$, $V_2 = 10\text{ V}$ for the pulse voltage source. Wisely select its pulse width so that you can clearly observe the responses of the RL circuit.



6. Measure the current $i(t)$ in the circuit and voltage $v(t)$ across the inductor. Then plot them. What did you find? Why?
7. Fill the simulation results in Table 2

Table 2 Time Constant of RL Circuits

Resistance (Ω)	Inductance (mH)	Calculated Time Constant	Measured Time Constant
10	5		
10	10		
10	30		

Explain your results shown in the table above.

Questions and Conclusions

- Summarize your findings and explanations in response to the questions posed in this lab.