

ENGR 065 Electric Circuits

Lecture 10b: Maximum Power Transfer and Superposition



Today's Topics

- ▶ Maximum power transfer
 - under what condition that loads can obtain maximum power transferred from sources.
- ▶ The superposition principle
 - can only be applied to linear circuits

Covered in Sections 4.12 and 4.13

Power Transfer Calculation

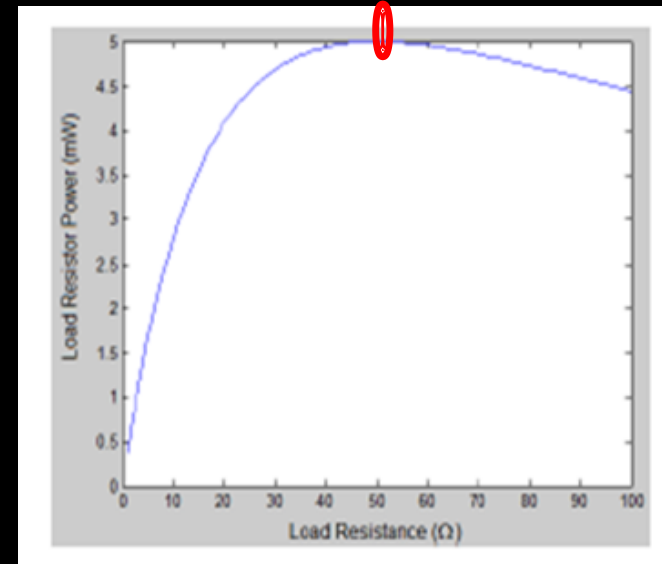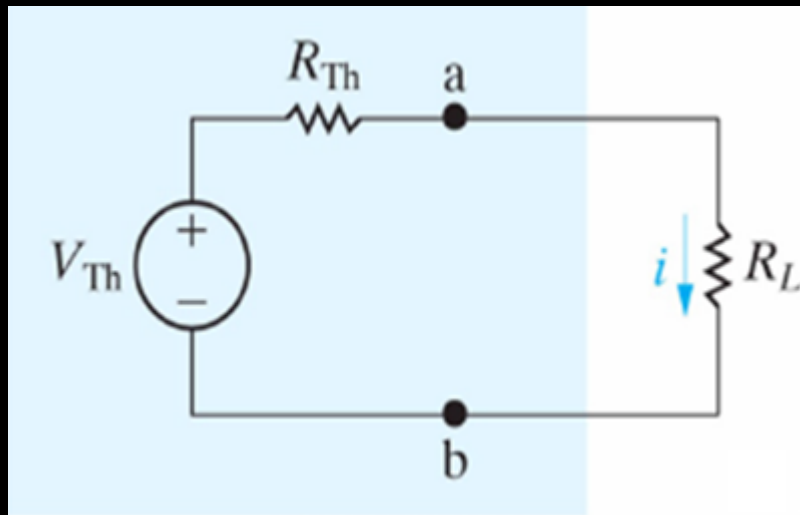The problem is to determine the value of R_L that permits maximum power delivery to R_L .



The power dissipated by R_L is

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

Maximum Power Transfer Calculation

Let $\frac{dp}{dR_L} = 0$, we have

$$\frac{dp}{dR_L} = \frac{d\left[\left(\frac{V_{Th}}{R_{Th} + R_L}\right)^2 R_L\right]}{dR_L} = V_{Th}^2 \frac{(R_{Th} + R_L)^2 - 2(R_{Th} + R_L)R_L}{(R_{Th} + R_L)^4} = 0$$


$$(R_{Th} + R_L)^2 - 2(R_{Th} + R_L)R_L = 0$$

$$R_L = R_{Th}$$

Which means when the load resistance is equal to the Thévenin equivalent resistance, the maximum power is transferred to the load.


Maximum Power Transfer

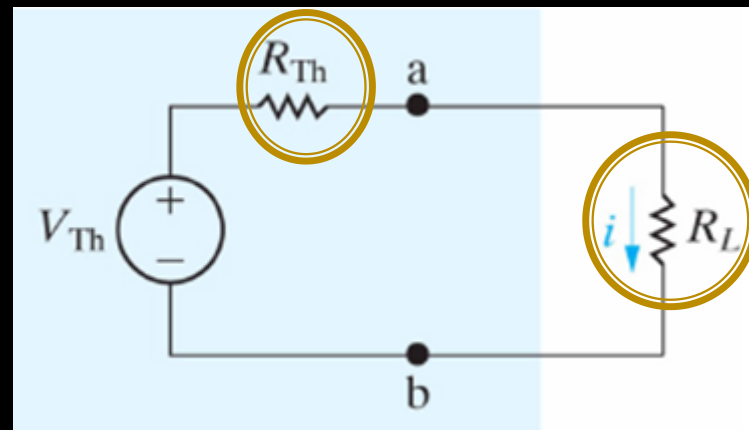- ▶ In an electrical system, maximum power transferred from a power source to a load is when the resistance of the load R_L is equal to the equivalent or internal resistance of the source, which is $R_L = R_{Th}$ or $R_L = R_{IN}$.
- ▶ The process to match $R_L = R_{Th}$ or $R_L = R_{IN}$ is called **resistance or impedance matching**.



The Maximum Power Delivered to Load

$$\begin{aligned} p_{max}|_{R_L=R_{Th}} &= \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \\ &= \left(\frac{V_{Th}}{R_L + R_L} \right)^2 R_L \\ &= \frac{V_{Th}^2}{4R_L^2} R_L \\ &= \frac{V_{Th}^2}{4R_L} \end{aligned}$$

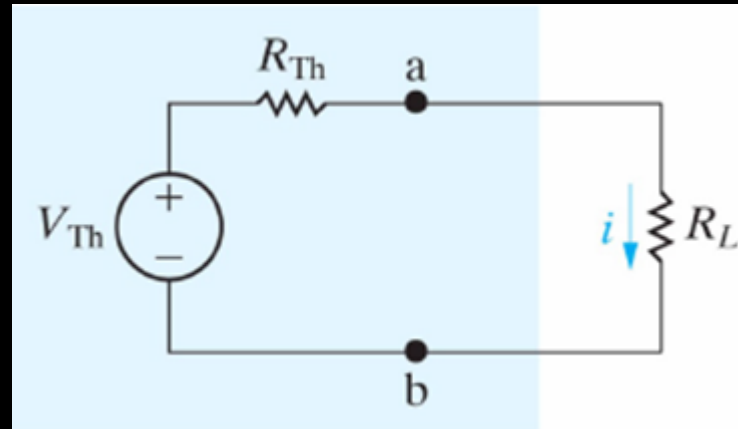


In addition, the power dissipated by **the equivalent resistor** (R_{Th} , R_N or R_{IN}) is same as the power absorbed by the load.

$$p_{\textcircled{R_{Th}}} = p_{R_L} = \frac{V_{Th}^2}{4R_L}$$

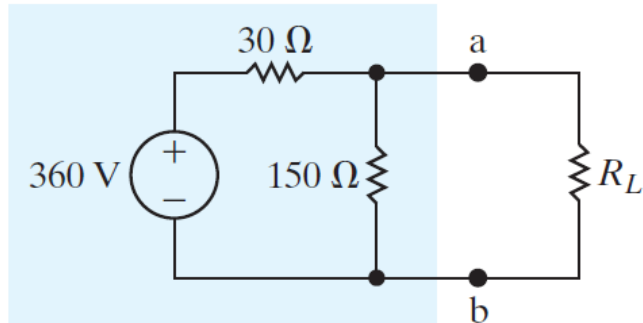Example #1

For the circuit shown on the left, find the value of R_L that results in the maximum power being transferred to R_L and this maximum power.



1. Find R_{Th}



$$R_{Th} = \frac{30 \times 150}{30 + 150} = 25 \Omega$$

$$R_L = R_{Th} = 25 \Omega$$

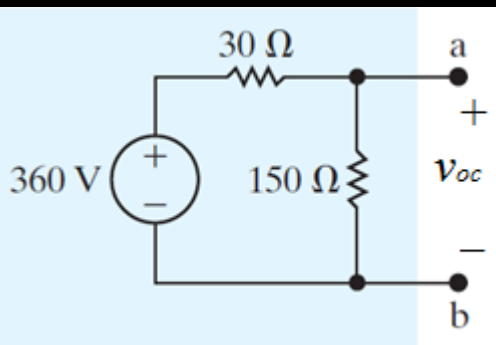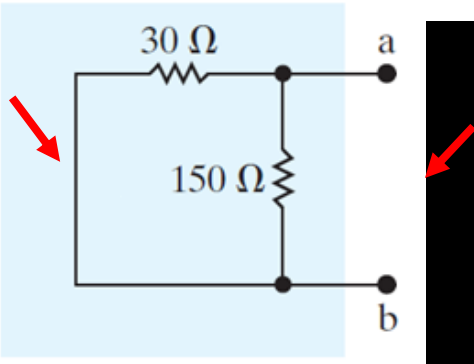
2. Find V_{Th}

$$V_{Th} = v_{oc} = \frac{360 \times 150}{30 + 150} = 300 V$$

$$p_{max} = \frac{V_{Th}^2}{4R_L} = \frac{300^2}{4 \times 25} = 900 W$$



Example #1 – cont'

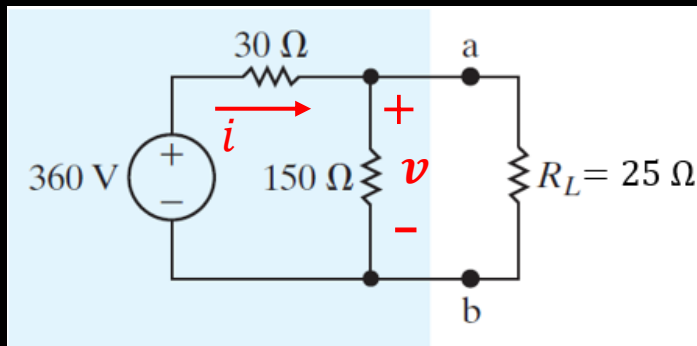

Let's find the power associated with all elements in the circuit.

$$i = \frac{360}{30 + \frac{150 \times 25}{150 + 25}} = 7 \text{ A}$$

$$p_{360 \text{ V}} = -7 \times 360 = -2520 \text{ W}$$

$$p_{30} = i^2 \times R = 7^2 \times 30 = 1470 \text{ W}$$

$$v = 360 - 30 \times 7 = 150 \text{ V}$$

$$p_{150} = \frac{150^2}{150} = 150 \text{ W}$$

$$p_{25} = \frac{150^2}{25} = 900 \text{ W}$$

What do the results tell you?


The Superposition Principle

- ▶ The superposition principle can only be applied to linear circuits (systems).
- ▶ What is a linear circuit or system?
- ▶ If a circuit or system is linear, it must hold the following two properties:
 - **Homogeneity:** $y(ax) = ay(x)$
 - **Additivity:** $y(x_1 + x_2 + \cdots + x_n) = y(x_1) + y(x_2) + \cdots + y(x_n)$


The Superposition Principle

If a circuit (system) is linear (homogeneity + additivity), we have
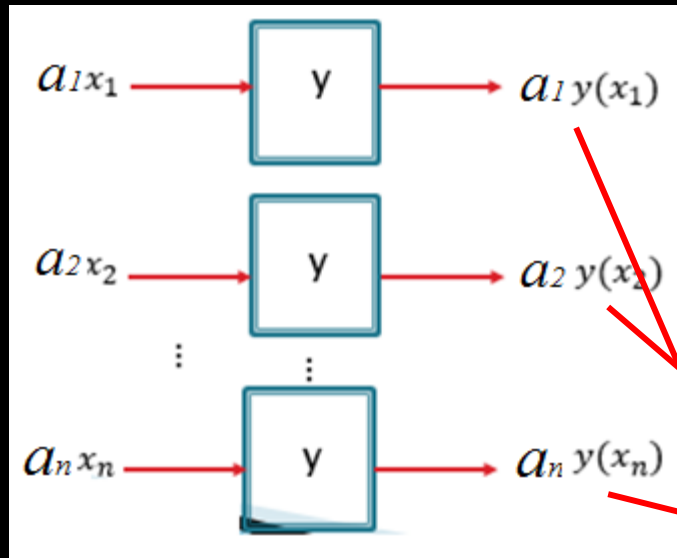
$$y(ax) = ay(x) \text{ and } y(x_1 + x_2 + \cdots + x_n) = y(x_1) + y(x_2) + \cdots + y(x_n)$$



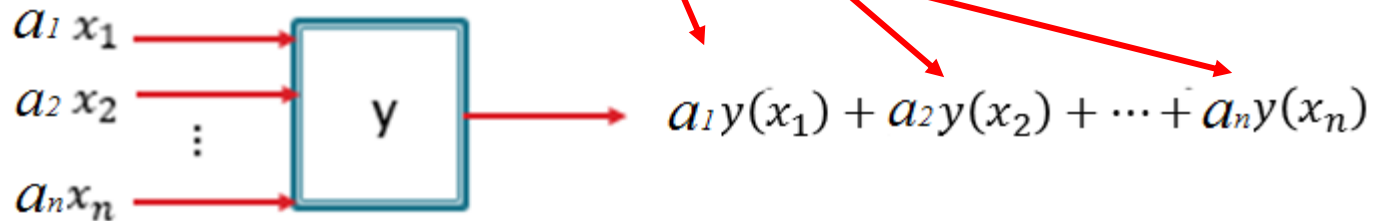Whenever a linear circuit is driven by more than one **independent** sources, the response caused by these multiple sources is the sum of the individual responses.



Steps in Applying the Superposition Principle

1. If there are multiple **independent** sources in a circuit, keep **ONE** independent source in the circuit and remove all other **independent** sources. The removed voltage sources are replaced with short circuits and current sources replaced with open circuits.
2. Find the response driven by the **kept** independent source.
3. Repeat Step 1 and 2 for **each** independent source.
4. Algebraically **add** the responses driven by all the individual independent sources found in Steps 1 to 3 above.

Example #2

Find the current i

1. There are two independent sources in the circuit.

2. Keep the 10V voltage source in the circuit and remove the 2A current source.

3. Find i_1 . $(2+10)//5+1 = 4.53 \Omega$

$$i_a = \frac{10}{4.53} = 2.21 \text{ A}$$




$$i_1 = \frac{i_a \times 5}{5 + 12} = 0.65 \text{ A (current division)}$$

4. Keep the 2A current source in the circuit and remove the 10V voltage source.




$$1//5+2 = 2.83 \Omega$$

$$i_2 = -\frac{2 \times 10}{10 + 2.83} = -1.56 \text{ A (current division)}$$
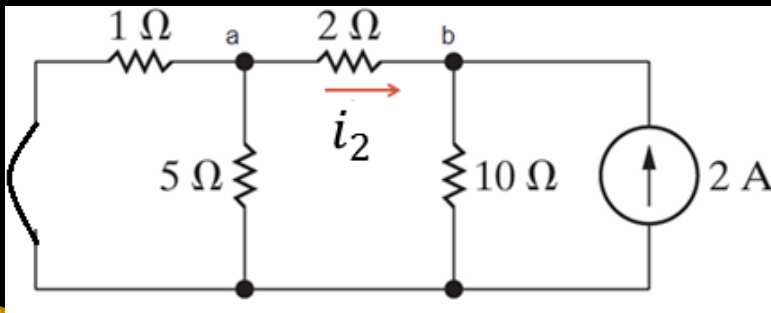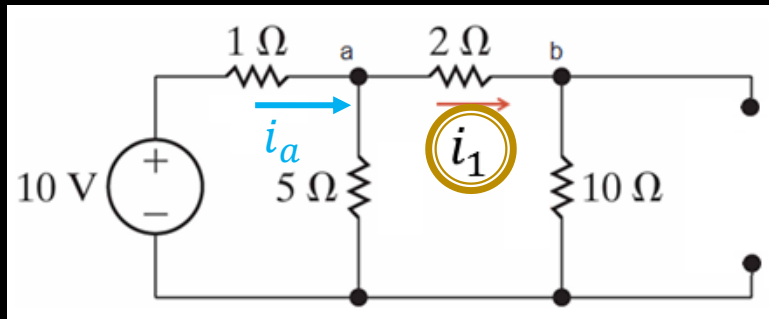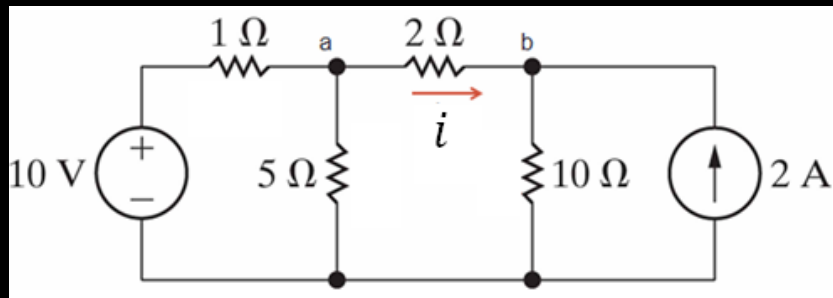
$$i = i_1 + i_2 = 0.65 - 1.56 = -0.91 \text{ A}$$



Example #3 (P.4.20)

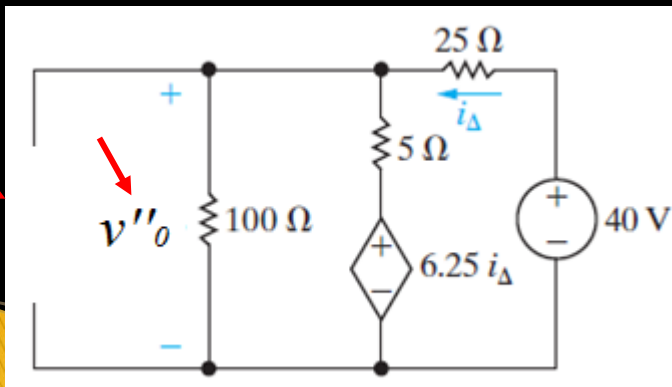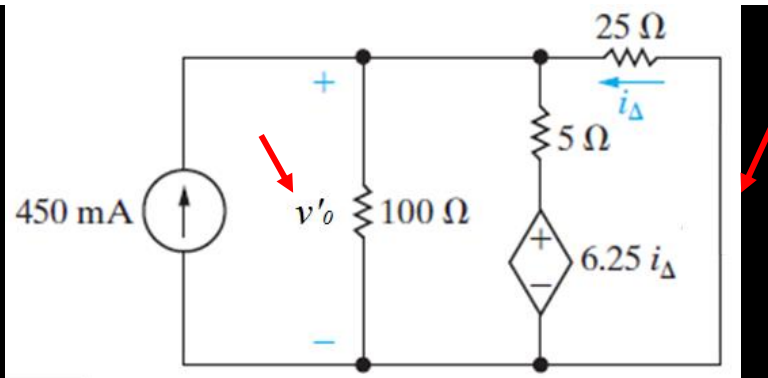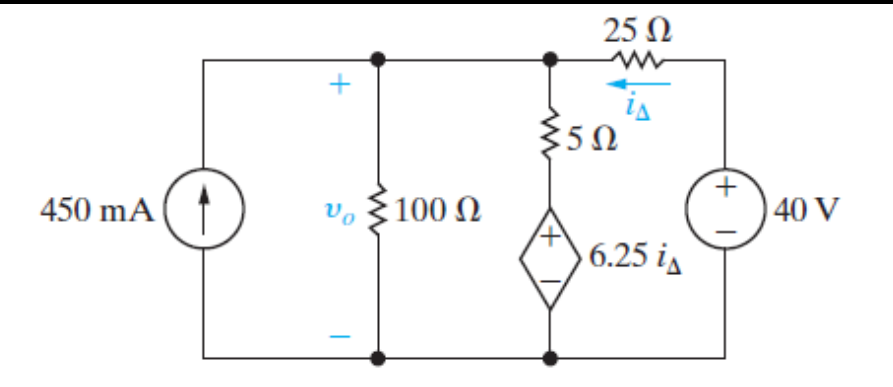

Use the superposition to find v_o .

1. Remove the 40 V voltage source
2. Use node-voltage method to find v'_o .

$$-0.45 + \frac{v'_o}{100} + \frac{v'_o - 6.25i_\Delta}{5} + \frac{v'_o}{25} = 0$$

$$i_\Delta = -\frac{v'_o}{25} \text{ (Ohm's law)}$$

Solve above equations for v'_o , we have:

$$v'_o = 1.5 \text{ V}$$

3. Remove the 450 mA current source

4. Use node-voltage method to find v''_o .

$$\frac{v''_o}{100} + \frac{v''_o - 6.25i_\Delta}{5} + \frac{v''_o - 40}{25} = 0$$

$$i_\Delta = -\frac{v''_o - 40}{25}$$

Solve above equations for v''_o , we have:

$$v''_o = 12 \text{ V}$$

$$5. v_o = v'_o + v''_o = 1.5 + 12 = 13.5 \text{ V}$$

Summary

- ▶ In this chapter, we learned four important techniques that can be used in circuit analysis:
 1. Node-voltage and mesh-current methods
 2. Source transformations
 3. Thévenin and Norton equivalents
 4. Superposition

In the next lecture, we will discuss the applications of these techniques:

The operational amplifier