

ENGR 065 Electric Circuits

Lecture: Midterm Review

Today's Topics

- ▶ Review the Midterm concepts taught thus far
 - **Major Topics**
 - Variables:
 - Three Laws:
 - Circuit Analysis Techniques:
 - Basic Equations:
 - Basic Concepts:
- ▶ Go through sample problems as class exercise

Midterm Review

Variables:

- Voltage
- Current
- Resistance
- Power
- Energy

Three Laws:

- Ohm's Law
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)

Circuit Analysis Techniques:

- KCL and KVL
- Resistance combinations
- Node-voltage and mesh-current
- Source transformations
- Thévenin and Norton Theorem


Basic Equations and Concepts:

- Power and energy in resistors
- Passive sign convention
- Ideal circuit elements: passive/active
- Ideal independent sources: volt/current
- Dependent sources: (careful w/ units)
 - Voltage controlled (volt/current)
 - Current controlled (volt/current)
- Divider circuits:
 - Voltage/current
- Open circuits:
 - $R = \infty$, no loads, switch (off state)
- Short circuits:
 - $R = 0$ ($V = 0$), wires, switch (on state)
- Maximum power transfer
- Equivalent circuits
 - Series/parallel resistors
 - Series/parallel volt/current sources
 - Source transformations
 - Thévenin/Norton
- Superposition principle

Sample Questions

1) The equivalent resistance seen by the terminals **a** and **b** is

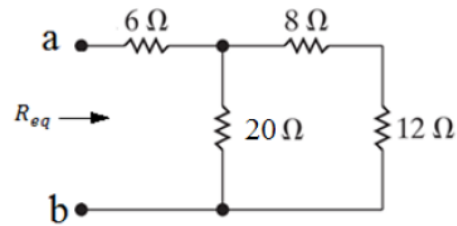
- A. $4\ \Omega$
- B. $6\ \Omega$
- C. $8\ \Omega$
- D. $16\ \Omega$



Sample Questions

2) The power associated with $10\ \Omega$ resistor is

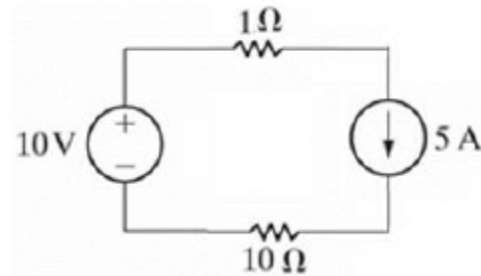
- A. 25 W
- B. - 25 W
- C. 250 W
- D. - 250 W



Sample Questions

3) The power associated with 10 V voltage source is

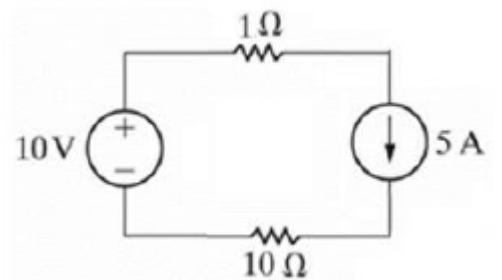
- A. 50 W
- B. - 50 W
- C. 25 W
- D. - 25 W



Sample Questions

4) The current i_x is


- A. 1 A
- B. -1 A
- C. 3 A
- D. -3 A

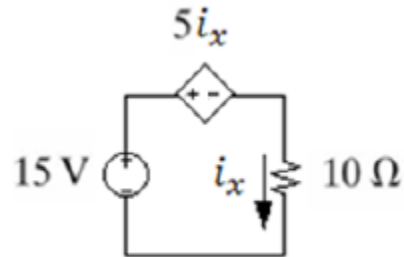

Sample Questions

5) The voltage v_x is


- A. 5 V
- B. 10 V
- C. 15 V
- D. 20 V

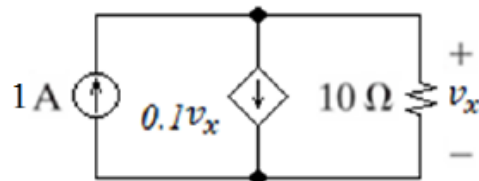

Sample Questions

6) The node voltage equation at node 1 in the circuit to the right is

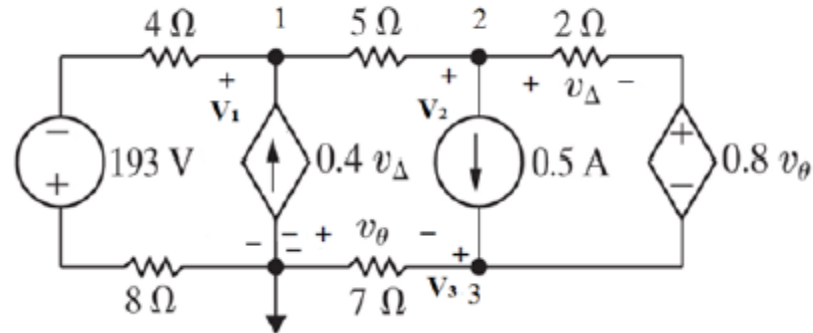
- A. $\frac{v_1 - 193}{12} - 0.4v_\Delta + \frac{v_1 - v_2}{5} = 0$
- B. $\frac{v_1 - 193}{4} + 0.4v_\Delta + \frac{v_1 - v_2}{5} = 0$
- C. $\frac{v_1 + 193}{12} - 0.4v_\Delta + \frac{v_1 - v_2}{5} = 0$
- D. $\frac{v_1 + 193}{4} + 0.4v_\Delta + \frac{v_1 - v_2}{5} = 0$



Sample Questions

7) The node voltage equation at node 2 in the circuit to the right is

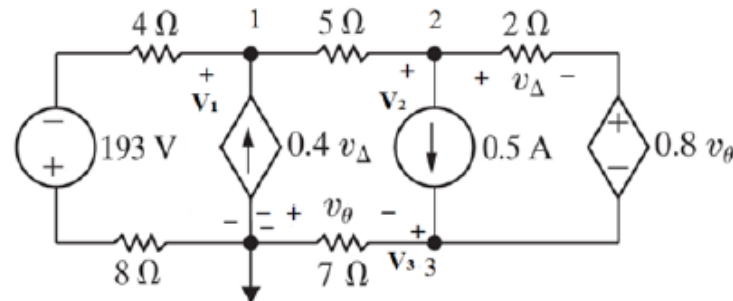
- A. $\frac{v_2 - v_1}{5} + 0.5 + \frac{v_2 - 0.8v_\theta - v_3}{2} = 0$
- B. $\frac{v_1 - v_2}{5} - 0.5 + \frac{v_2 - 0.8v_\theta + v_3}{2} = 0$
- C. $\frac{v_2 - v_1}{5} - 0.5 + \frac{v_2 - 0.8v_\theta}{2} = 0$
- D. $\frac{v_1 - v_2}{5} + 0.5 + \frac{v_2 - 0.8v_\theta}{2} = 0$



Sample Questions

8) The node voltage equation at node 3 in the circuit to the right is

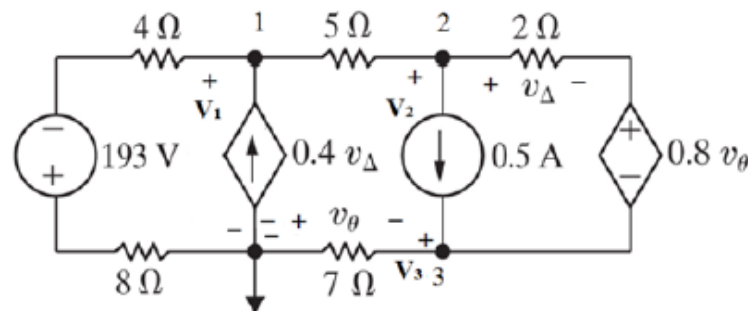
- A. $\frac{V_2}{7} + 0.5 + \frac{V_2 - 0.8v_\theta - V_2}{2} = 0$
- B. $\frac{V_2}{7} - 0.5 + \frac{V_2 - 0.8v_\theta - V_2}{2} = 0$
- C. $\frac{V_2}{7} - 0.5 + \frac{V_2 + 0.8v_\theta - V_2}{2} = 0$
- D. $\frac{V_2}{7} + 0.5 + \frac{V_2 + 0.8v_\theta - V_2}{2} = 0$



Sample Questions

9) The v_θ in the circuit to the right is equal to

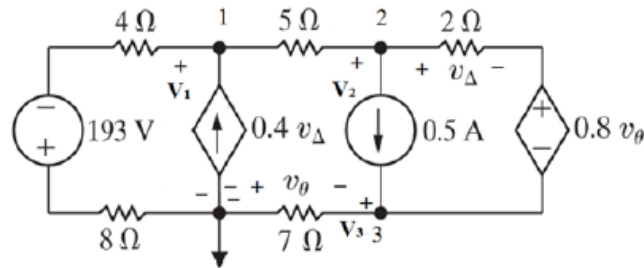
- A. $-V_1$
- B. $-V_2$
- C. $-V_3$
- D. 0



Sample Questions

10) The v_Δ in the circuit to the right is equal to

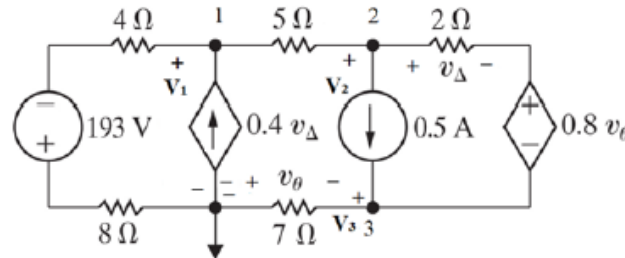
- A. $\frac{v_2 + 0.8v_\theta - v_3}{2}$
- B. $v_2 - 0.8v_\theta - v_3$
- C. $\frac{v_2 - 0.8v_\theta}{2}$
- D. $v_2 + 0.8v_\theta$



Sample Questions

11) The mesh-current equation of mesh a in the circuit to the right is

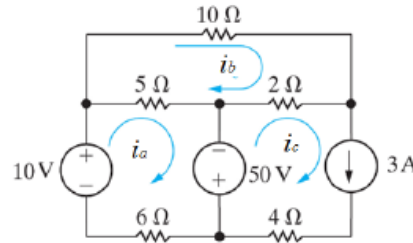
- A. $11i_a - 6i_b + 50 = 0$
- B. $11i_a - 5i_b - 50 = 0$
- C. $11i_a - 6i_b + 60 = 0$
- D. $11i_a - 5i_b - 60 = 0$



Sample Questions

12) The mesh-current equation of mesh **b** in the circuit to the right is

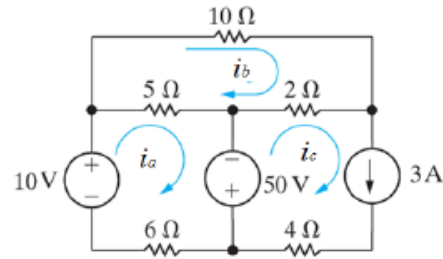
- A. $-5i_a + 17i_b - 2i_c = 0$
- B. $-2i_a - 17i_b - 5i_c = 0$
- C. $-5i_a + 10i_b - 2i_c = 0$
- D. $-2i_a - 10i_b - 5i_c = 0$



Sample Questions

13) The mesh-current equation of mesh c in the circuit to the right is

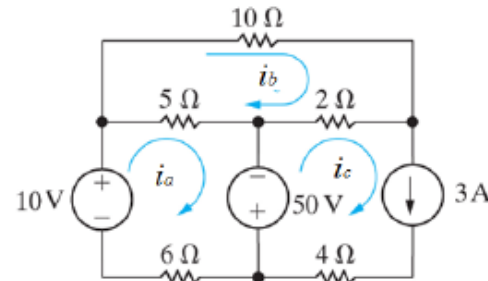
- A. $6i_c - 2i_b - 50 = 0$
- B. $6i_c - 2i_b + 50 = 0$
- C. $4i_c - 2i_b - 50 = 0$
- D. $i_c = 3\text{ A}$



Sample Questions

14) The Thévenin equivalent resistance at the terminals **a** and **b** in the circuit below is

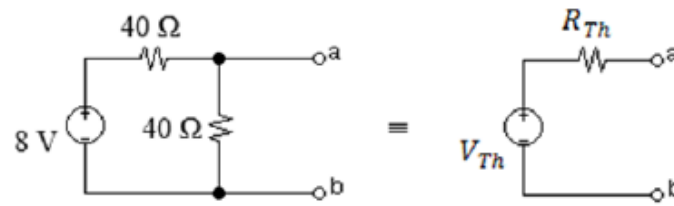
- A. $10\ \Omega$
- B. $20\ \Omega$
- C. $40\ \Omega$
- D. $80\ \Omega$



Sample Questions

15) The Thévenin equivalent voltage V_{Th} at the terminals a and b in the circuit below is


- A. 3 V
- B. -3 V
- C. 4 V
- D. -4 V

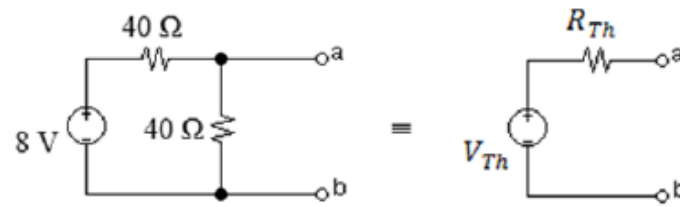

Sample Questions


16) The maximum power transferred to the R_L is

- A. 5 W
- B. 10 W
- C. 40 W
- D. 200 W

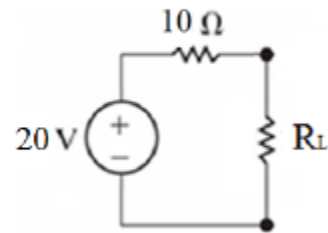


Sample Free Response Questions

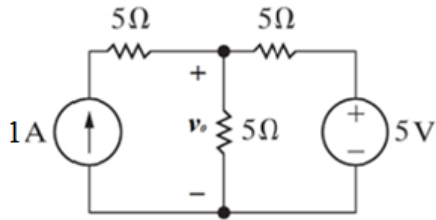1) Using the source transformation to find the voltage v_o in the circuit below



Sample Free Response Questions

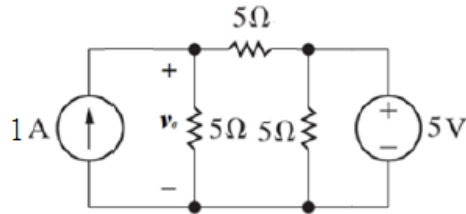2) Using the superposition principle method to find the voltage v_0 in the following circuit



Bonus Questions

Bonus question (10 pts/each)

In the circuit below, if it is only driven by the independent voltage source, $i_{\Delta} = 0.5 \text{ A}$. If it is only driven by the independent current source, $i_{\Delta} = -0.1 \text{ A}$. If the value of the voltage source is changed to 60 V and the value of the current source is changed to 8 A, and both sources are applied to the circuit, i_{Δ} is equal to

- A. 0.1 A
- B. 0.2 A
- C. 0.6 A
- D. 1.0 A

