

ENGR 065 Electric Circuits

Lecture 11: The Operational Amplifier



Today's Topics

- ▶ Operational amplifier terminals
- ▶ The **ideal** operational amplifier
- ▶ The inverting-amplifier circuit
- ▶ The summing-amplifier circuit
- ▶ The noninverting-amplifier circuit
- ▶ The difference-amplifier circuit
 - The common mode rejection ratio (CMRR)

Covered in Sections 5.1, 5.2, 5.3, 5.4, 5.5, and 5.6

Introductions

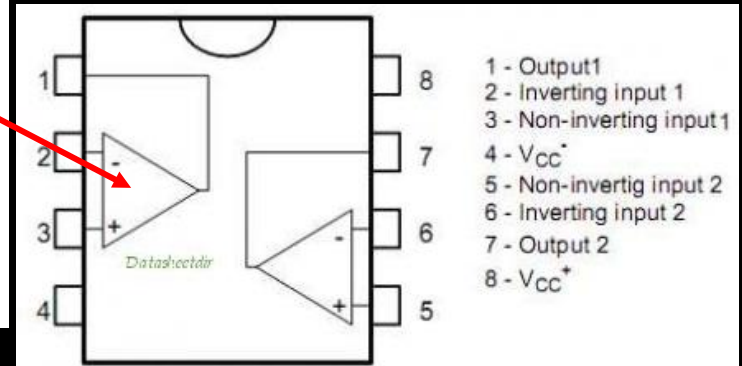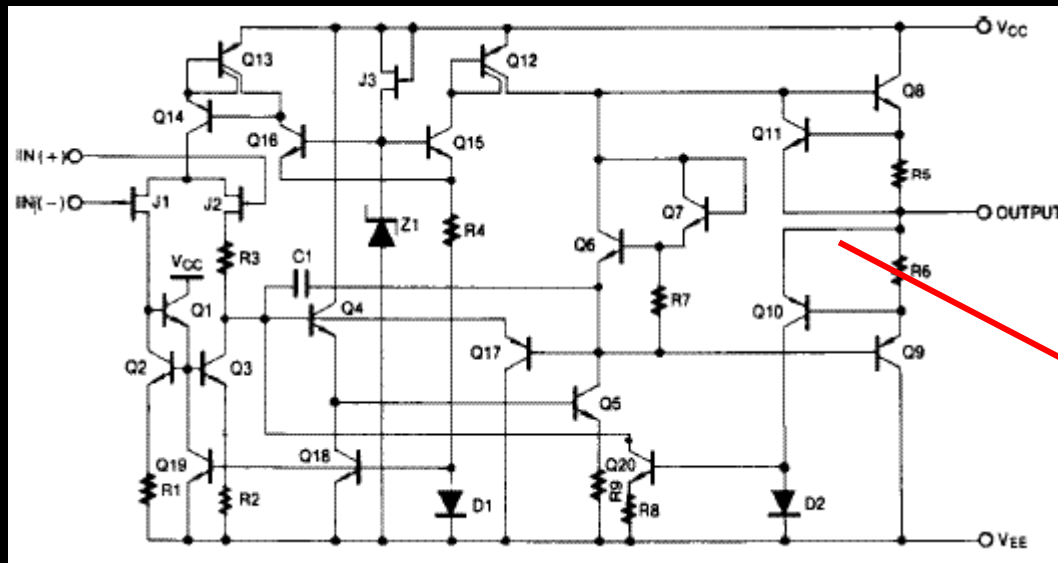Operational amplifiers (Op-amps) are made of many transistors, diodes, resistors and capacitors with integrated circuit technology.




Introduction

- Op-amps are the basic components used to build analog circuits.
- Most op-amps behave like voltage amplifiers. They take an input voltage and output a scaled version.
- The name “operational amplifier” comes from the fact that they were originally used to perform mathematical operations such as summing, subtracting, integration, and differentiation.
- The fabrication techniques of **I**ntegrated **c**ircuits make high-performance op-amps very cheap in comparison to older discrete devices.



Terminal Voltages and Currents

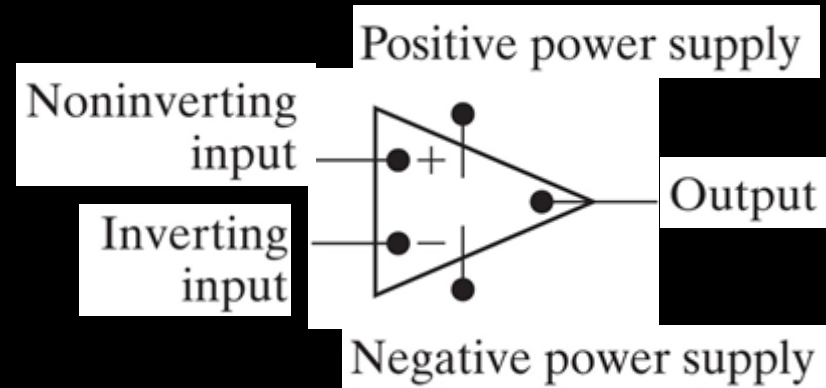2. There are five primary terminals:

- Inverting input
- Noninverting input
- Output
- Positive power supply
- Negative power supply



1. The circuit symbol for an op-amp

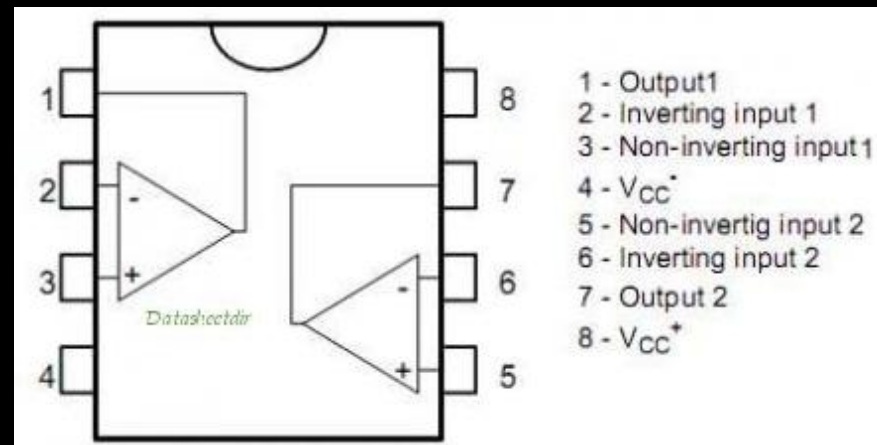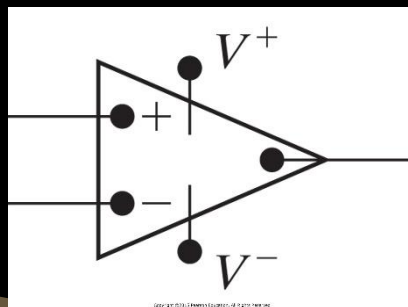


Terminal Voltages and Currents

3. Terminal voltage variables

v_n : the voltage between the inverting input terminal and the common(reference) node.

v_p : the voltage between the noninverting input terminal and the common node.

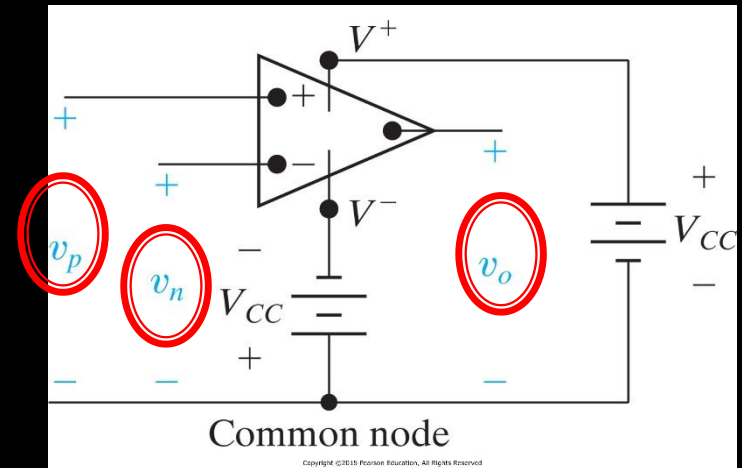v_o : the voltage between the output terminal and the common node.



4. Terminal current variables


i_n : the current into the inverting input terminal.

i_p : the current into the noninverting input terminal.


i_o : the current into the output terminal.

i_{c+} : the current into the positive power supply terminal.

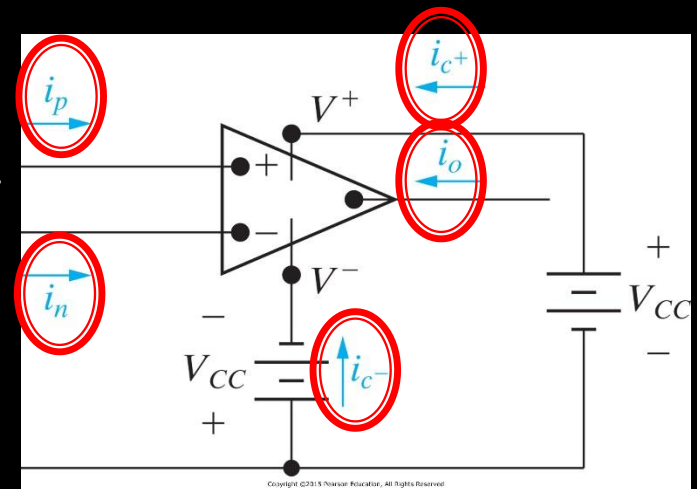
i_{c-} : the current into the negative power supply terminal.



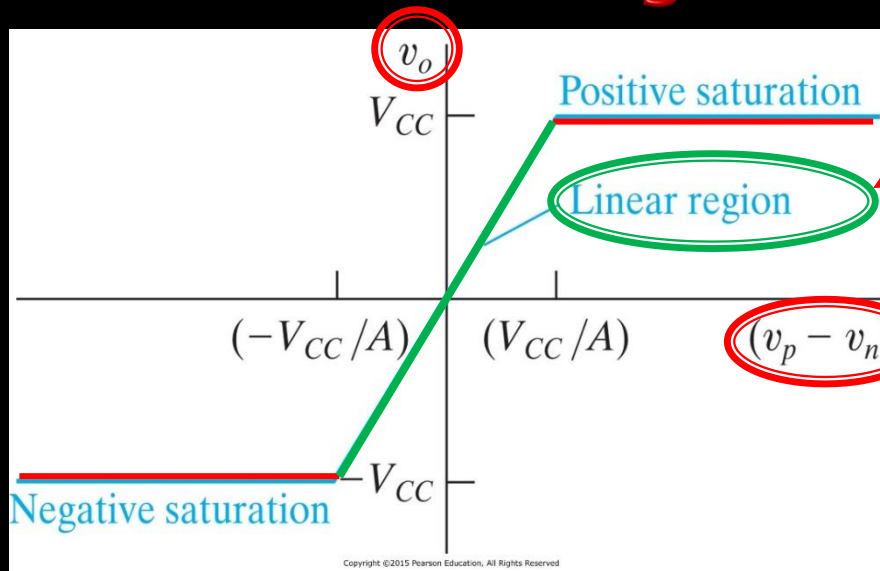Terminal Voltages and Currents ($A \neq \infty$)



This is the region we prefer

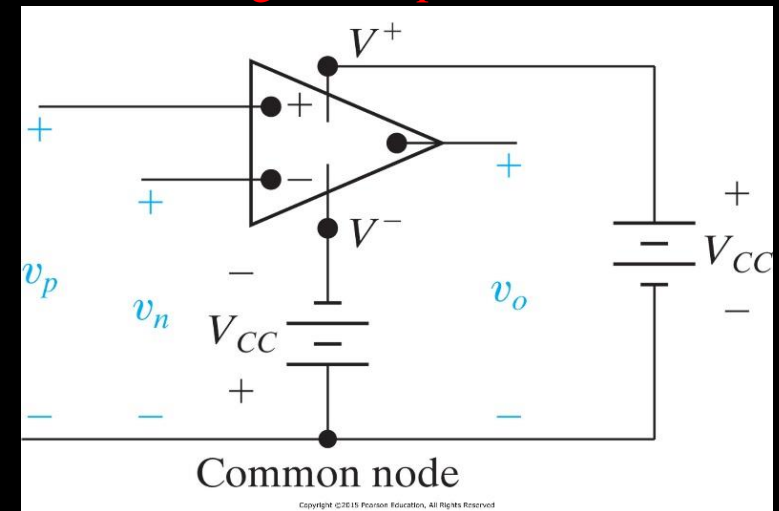

The output voltage of the op- amp is:

$$v_o = \begin{cases} -V_{CC} & A(v_p - v_n) < -V_{CC} \\ A(v_p - v_n) & -V_{CC} \leq A(v_p - v_n) \leq +V_{CC} \\ +V_{CC} & A(v_p - v_n) > +V_{CC} \end{cases}$$

where A is called the open-loop gain of the op amp.

The Constraints of Ideal Op-Amps

1. The input resistance is infinite

$$R_i = \infty$$


2. The output resistance is zero

$$R_o = 0$$

3. The open-loop gain is infinite

$$A = \infty$$

4. The frequency bandwidth is infinite

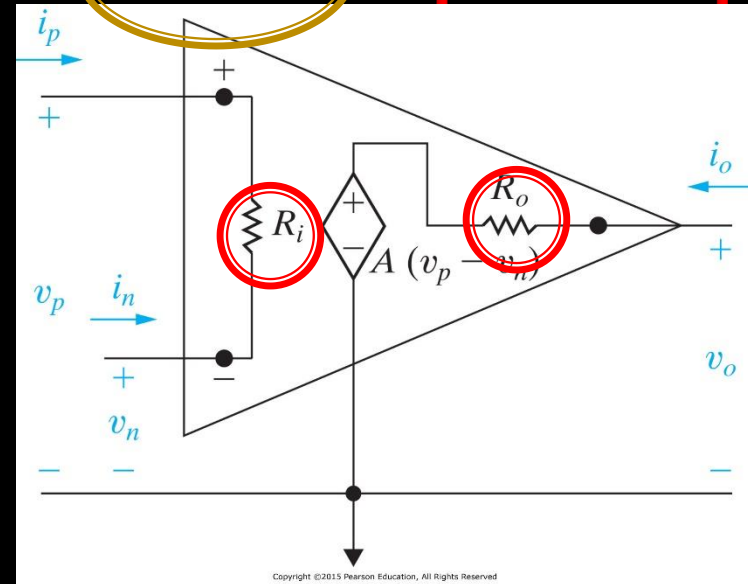

5. Input voltage constraint for **ideal** op-amps (virtual short)

$$v_p = v_n, v_p - v_n = 0 \quad (\text{because } A = \infty)$$

6. Input current constraint for ideal op amps

$$i_p = i_n = 0 \quad (\text{because } R_i = \infty)$$

7. From KCL, we know:


$$i_p + i_n + i_o + i_{c+} + i_{c-} = 0$$

Substituting the current constraint, we have:

$$i_o = -(i_{c+} + i_{c-})$$

The Inverting-Amplifier Circuit

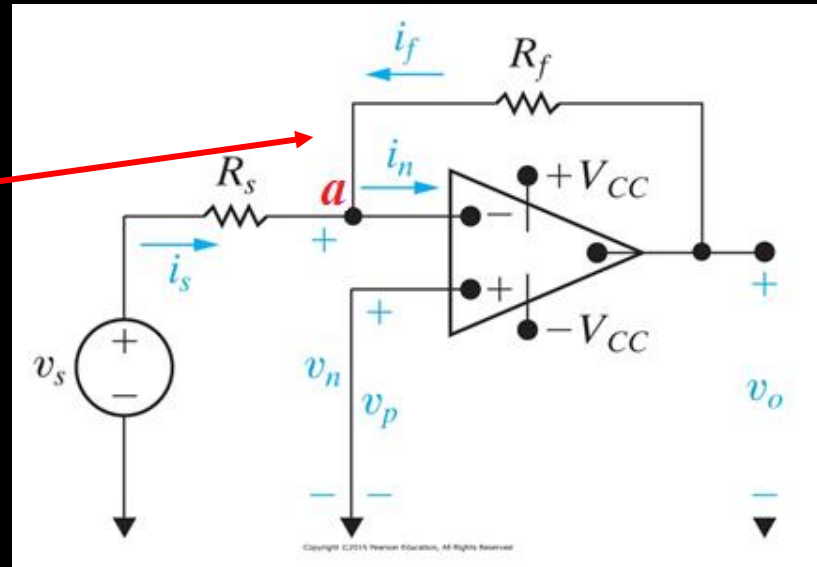The output signal is fed back from the output terminal to the inverting input terminal. This configuration is called **negative feedback connection**.



Because the noninverting terminal is connected to ground, $v_p = 0$, so $v_n = 0$

$$i_s = \frac{v_s - v_n}{R_s} = \frac{v_s}{R_s}, \quad i_f = \frac{v_o - v_n}{R_f} = \frac{v_o}{R_f}$$

Because $i_n = 0$, Applying KCL at node a , we know: $i_s + i_f = 0$, which means

$$\frac{v_s}{R_s} + \frac{v_o}{R_f} = 0,$$


so

$$v_o = -\frac{R_f}{R_s} v_s$$

$$G = \frac{v_o}{v_s} = -\frac{R_f}{R_s}$$

G is called the closed-loop gain of the op-amp.

The Summing-Amplifier Circuit

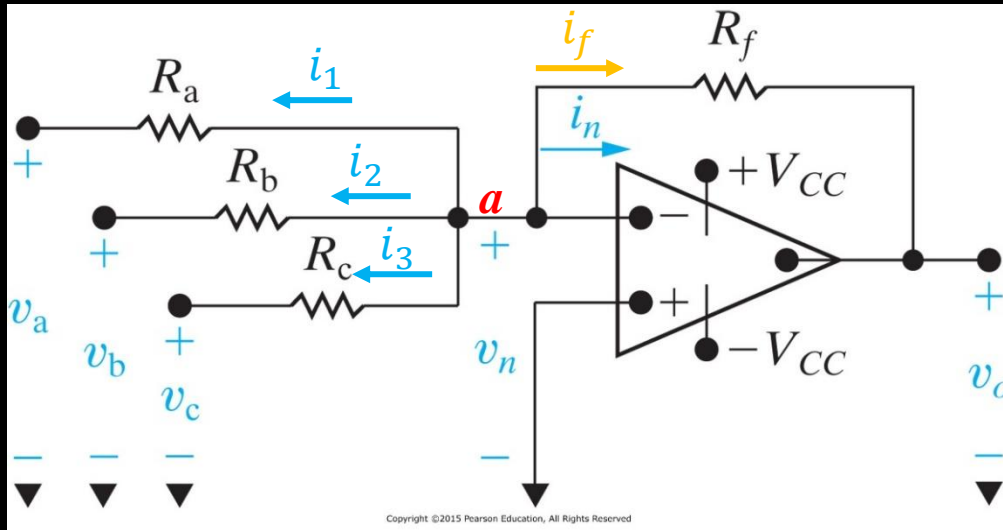


$$i_1 = \frac{v_n - v_a}{R_a}, \quad i_2 = \frac{v_n - v_b}{R_b}, \quad i_3 = \frac{v_n - v_c}{R_c}, \quad i_f = \frac{v_n - v_o}{R_f}, \quad i_n = 0, \quad v_n = v_p = 0$$

Applying KCL at node a ,
$$\frac{v_n - v_a}{R_a} + \frac{v_n - v_b}{R_b} + \frac{v_n - v_c}{R_c} + \frac{v_n - v_o}{R_f} + i_n = 0$$

$$v_o = - \left(\frac{R_f}{R_a} v_a + \frac{R_f}{R_b} v_b + \frac{R_f}{R_c} v_c \right)$$

The Noninverting-Amplifier Circuit

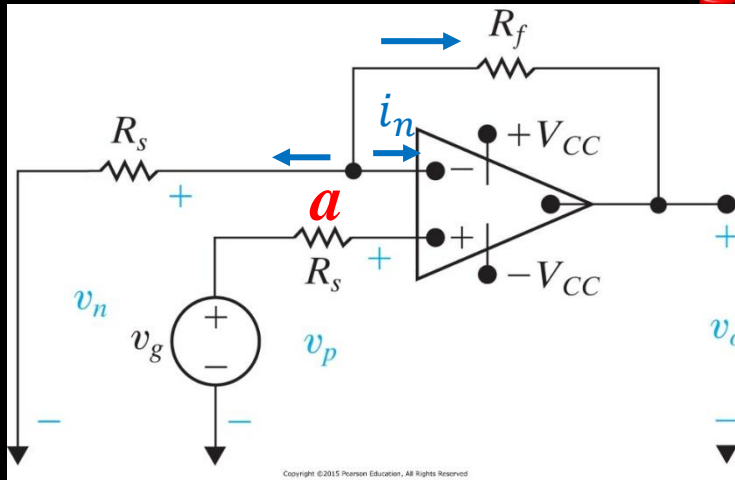

It is still a negative feedback connection. However, the source is connected to the non-inverting input terminal.

Because $i_p = 0$ (*ideal op - amp*), the voltage on R_s is zero and $v_p = v_g$. In addition, because $v_p = v_n$ (*ideal op - amp*), $v_n = v_g$.

As we know, at node a , $\frac{v_n - 0}{R_s} + \frac{v_n - v_o}{R_f} + i_n = 0$ and $i_n = 0$ (1)

From (1) $v_n = v_g = \frac{v_o R_s}{R_s + R_f}$

$$v_o = \frac{R_s + R_f}{R_s} v_g$$

$$G = \frac{R_s + R_f}{R_s}$$

The Difference-Amplifier Circuit

Applying KCL at node *a*

$$\frac{v_n - v_a}{R_a} + \frac{v_n - v_o}{R_b} + i_n = 0 \quad (1)$$

Because $i_p = i_n = 0$, applying the voltage division to the loop *b*

$$v_n = v_p = \frac{R_d}{R_c + R_d} v_b \quad (2)$$


Solving (1) and (2) for v_o ,

$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} v_b - \frac{R_b}{R_a} v_a \quad (3)$$

$$\text{If } \frac{R_a}{R_b} = \frac{R_c}{R_d},$$

$$v_o = \frac{R_b}{R_a} (v_b - v_a) \quad (4)$$

$$G = \frac{R_b}{R_a}$$

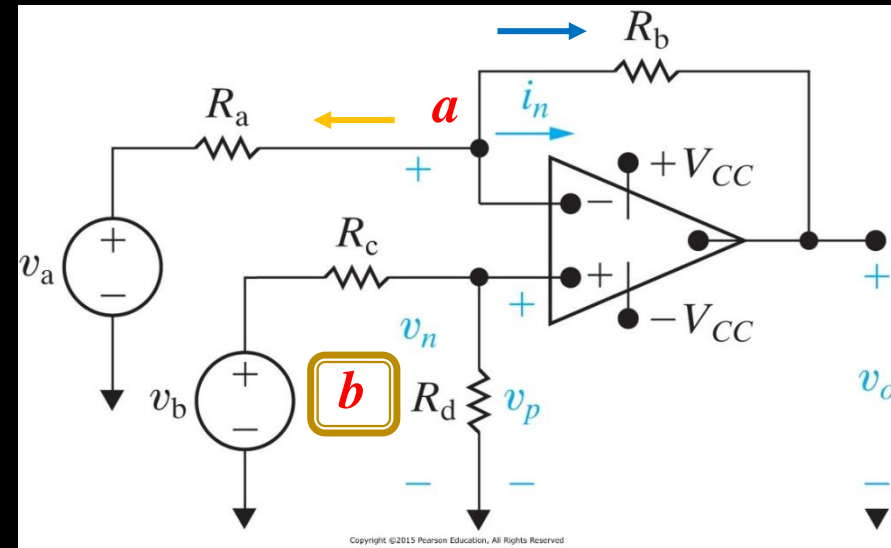

It is still a negative feedback connection. However, it has two sources, v_a and v_b .

The Difference-Amplifier Circuit


If we define the differential mode input

$$v_{dm} = v_b - v_a \quad (5)$$

Also, the common mode input is:

$$v_{cm} = (v_a + v_b)/2 \quad (6)$$

From (5) and (6), we have :

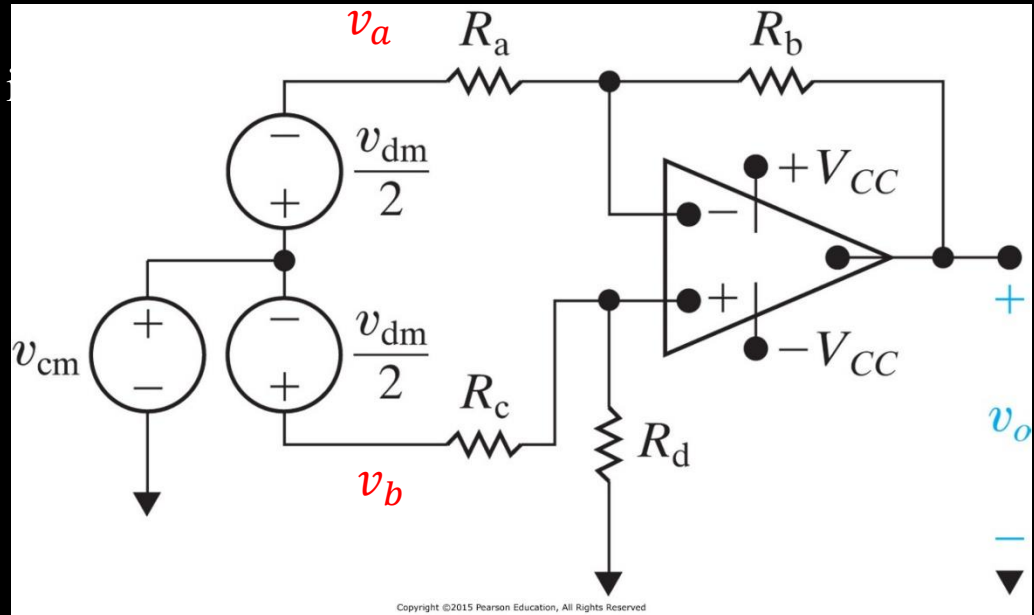


$$v_a = v_{cm} - \frac{1}{2}v_{dm}, \quad (7) \quad v_b = v_{cm} + \frac{1}{2}v_{dm} \quad (8)$$

The Difference-Amplifier Circuit

Substituting (7) and (8) into (3) , we have:

$$v_o = \frac{R_a R_d - R_b R_c}{R_a(R_c + R_d)} v_{cm} + \frac{R_d(R_a + R_b) + R_b(R_c + R_d)}{2R_a(R_c + R_d)} v_{dm}$$

$$= A_{cm} v_{cm} + A_{dm} v_{dm}$$

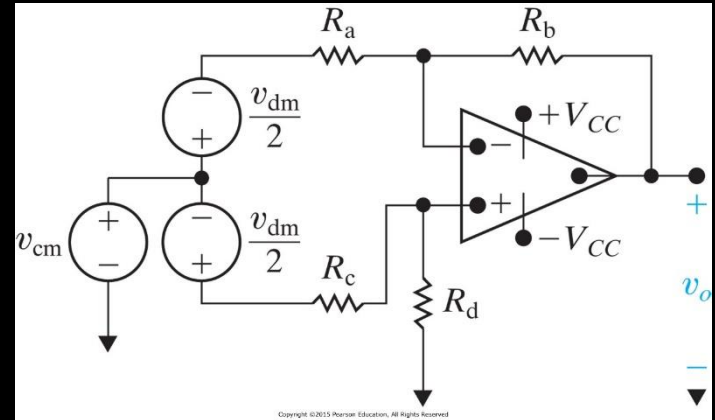

Where $A_{cm} = \frac{R_a R_d - R_b R_c}{R_a(R_c + R_d)}$ (9) is called the **common mode gain**

$A_{dm} = \frac{R_d(R_a + R_b) + R_b(R_c + R_d)}{2R_a(R_c + R_d)}$ (10) is called the **differential mode gain**

If $R_a = R_c$ and $R_b = R_d$,

$$v_o = 0v_{cm} + \frac{R_b}{R_a} v_{dm} = \frac{R_b}{R_a} v_{dm} \quad (11)$$


The Common Mode Rejection Ratio(CMRR)

Let's assume $\frac{R_a}{R_b} = (1 - \epsilon) \frac{R_c}{R_d}$, which means the resistance mismatches. Let us choose

$$R_a = (1 - \epsilon) R_c, R_b = R_d \quad (12)$$

$$\text{or } R_d = (1 - \epsilon) R_b, R_a = R_c \quad (13)$$

Substituting (13) into (9)

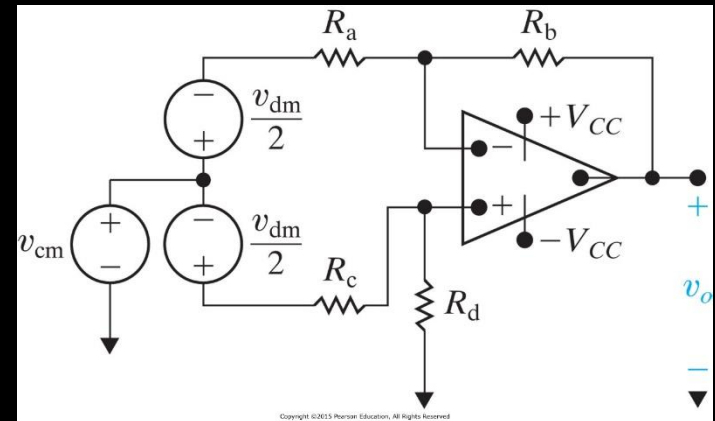

$$\begin{aligned} A_{cm} &= \frac{R_a(1 - \epsilon) R_b - R_b R_a}{R_a[R_a + (1 - \epsilon) R_b] - \epsilon R_b} \\ &= \frac{-\epsilon R_b}{R_a + (1 - \epsilon) R_b} \approx \frac{-\epsilon R_b}{R_a + R_b} \end{aligned}$$

The Common Mode Rejection Ratio

Substituting (13) into (10), we have

$$\begin{aligned} A_{dm} &= \frac{(1 - \epsilon) R_b (R_a + R_b) + R_b (R_c + (1 - \epsilon) R_b)}{2 R_a [R_c + (1 - \epsilon) R_b]} \\ &= \frac{R_b}{R_a} \left[1 - \frac{\epsilon/2 R_a}{R_a + (1 - \epsilon) R_b} \right] \approx \frac{R_b}{R_a} \left[1 - \frac{\epsilon/2 R_a}{R_a + R_b} \right] \end{aligned}$$


The common mode rejection ratio is defined as

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{\frac{R_b}{R_a} \left[1 - \frac{\epsilon/2 R_a}{R_a + R_b} \right]}{\frac{-\epsilon R_b}{R_a + R_b}} \right| \approx \left| \frac{1 + R_b/R_a}{-\epsilon} \right|$$

CMRR can be used to measure how excellent a difference amplifier circuit is. The larger the CMRR, the better the difference op-amp performs.

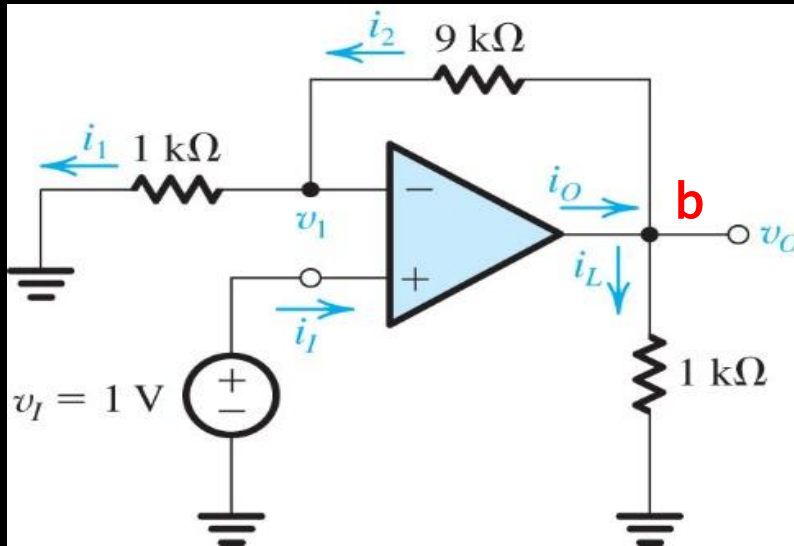Example #1

For the circuit below, find i_I , v_1 , i_1 , i_2 , v_0 , i_L , and i_0 .



$$i_I = 0$$

$$v_1 = v_I = 1 \text{ V}$$

$$i_1 = \frac{v_1}{1000} = 1 \text{ mA}$$

$$i_2 = i_1 = 1 \text{ mA}$$

$$\text{from } \frac{v_0 - v_1}{9000} = i_2 = 1 \text{ mA}$$


$$v_0 = 10 \text{ V}$$

At node b, applying KCL:

$$i_L + i_2 = i_0, \quad \text{So, } i_0 = 10 + 1 = 11 \text{ mA}$$

$$i_L = \frac{v_0}{1000} = 10 \text{ mA}$$

Example #2

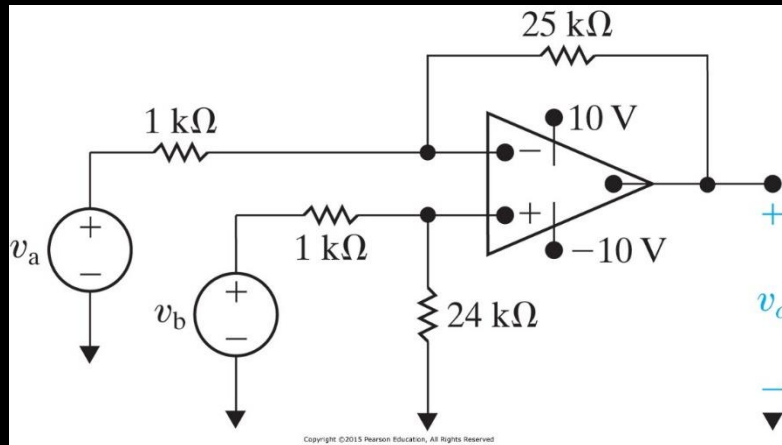

In the difference amplifier on the left, find

(a) The differential mode gain

(b) The common mode gain

(c) The CMRR

$$R_a = 1 \text{ k}\Omega, \quad R_b = 25 \text{ k}\Omega$$

$$R_c = 1 \text{ k}\Omega \quad R_d = 24 \text{ k}\Omega$$

$$A_{dm} = \frac{R_d(R_a + R_b) + R_b(R_c + R_d)}{2R_a(R_c + R_d)} = \frac{24(1 + 25) + 25(1 + 24)}{2 \times 1 \times (1 + 24)} = 24.98$$

$$A_{cm} = \frac{R_a R_d - R_b R_c}{R_a(R_c + R_d)} = \frac{1 \times 24 - 25 \times 1}{1 \times (1 + 24)} = -0.04$$

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{24.98}{-0.04} \right| = 624.5$$

Summary

- ▶ In this lecture, a simplified model is used to analyze an op-amp. The op-amp is considered as an ideal op-amp, which means it has infinite input resistance, infinite open-loop gain, and zero output resistance.
- ▶ The inverting, summing, noninverting, and difference amplifier are discussed.
- ▶ The common mode rejection mode(CMRR) is introduced. An ideal difference amplifier has an infinite CMRR.

In the next lecture, we will discuss:

1. The inductor and inductance
2. The capacitor and capacitance